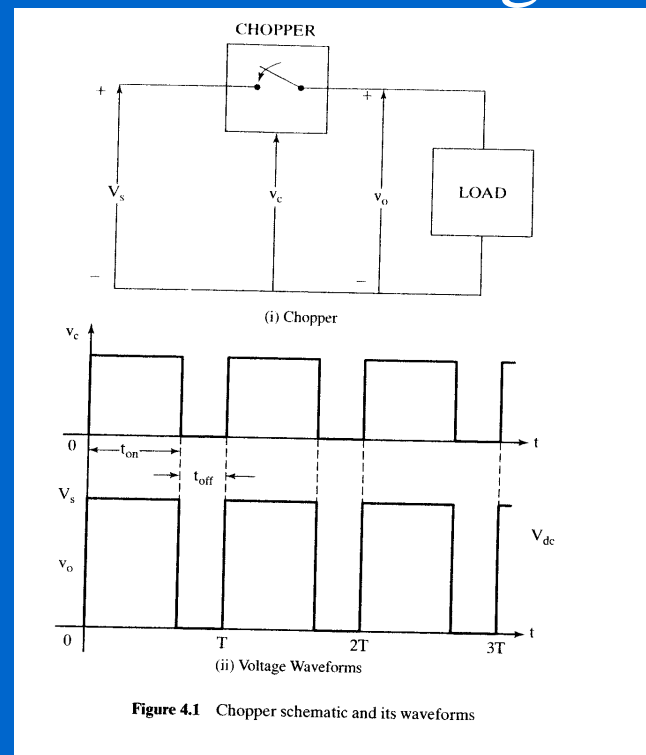


## 4 Chopper-Controlled DC Motor Drive

- Chopper: The variable dc voltage is controlled by varying the on- and off-times of a converter.
- Fig. 4.1 is a schematic diagram of the chopper.



- 
- 
- 

- Its frequency of operation is

$$f_c = \frac{1}{(t_{on} + t_{off})} = \frac{1}{T}$$

and its duty cycle is defined as

$$d = \frac{t_{on}}{T}$$

- Assuming that the switch is ideal, the average output is

$$V_{dc} = \frac{t_{on}}{T} V_s = dV_s$$

- varying the duty cycle changes the output voltage.

- 
- 
- 

- The duty cycle  $d$  can be changed in two ways:

- (i) varying the on-time (constant switching frequency).

- (ii) varying the chopping frequency.

- Constant switching frequency has many advantages in practice.

- 
- 
- 

## 4.3 Four-Quadrant Chopper Circuit

- Fig. 4.2 is the chopper circuit with transistor switches.


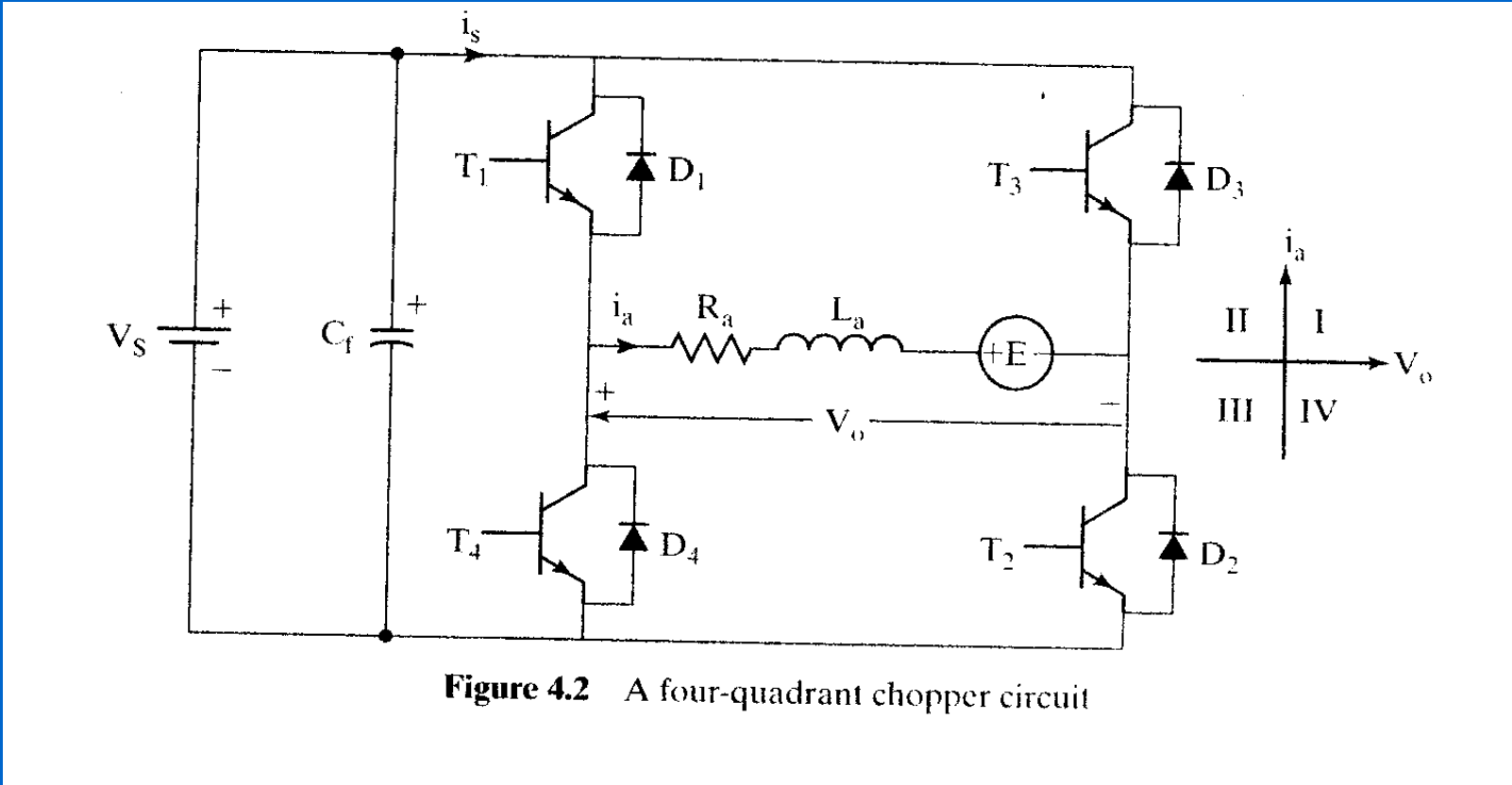



Figure 4.2 A four-quadrant chopper circuit

- 
- 
- 
- Fig. 4.3 is first-quadrant operation.

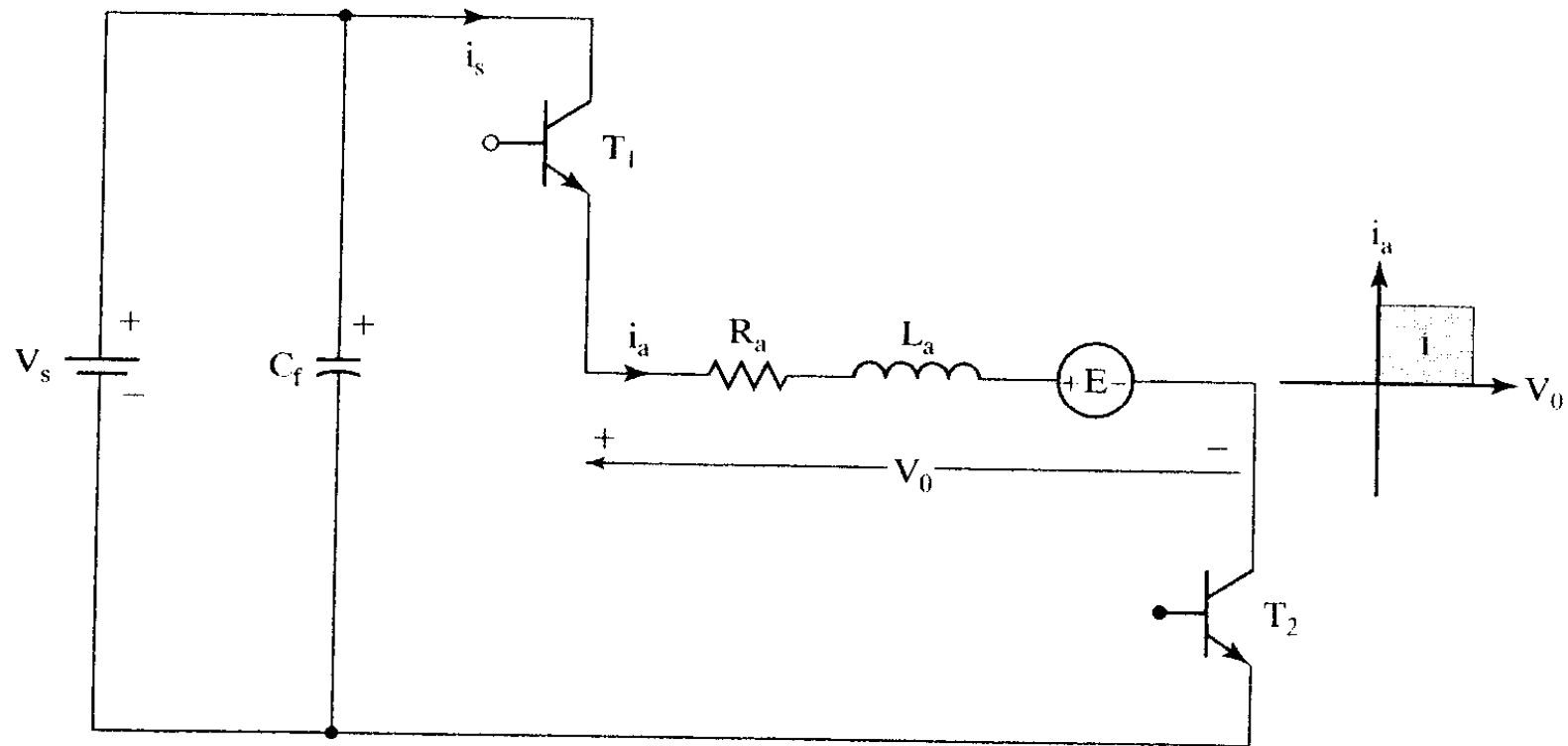


**Figure 4.3** First-quadrant operation with positive voltage and current in the load

- Fig. 4.4 is first-quadrant operation with zero voltage across the load.

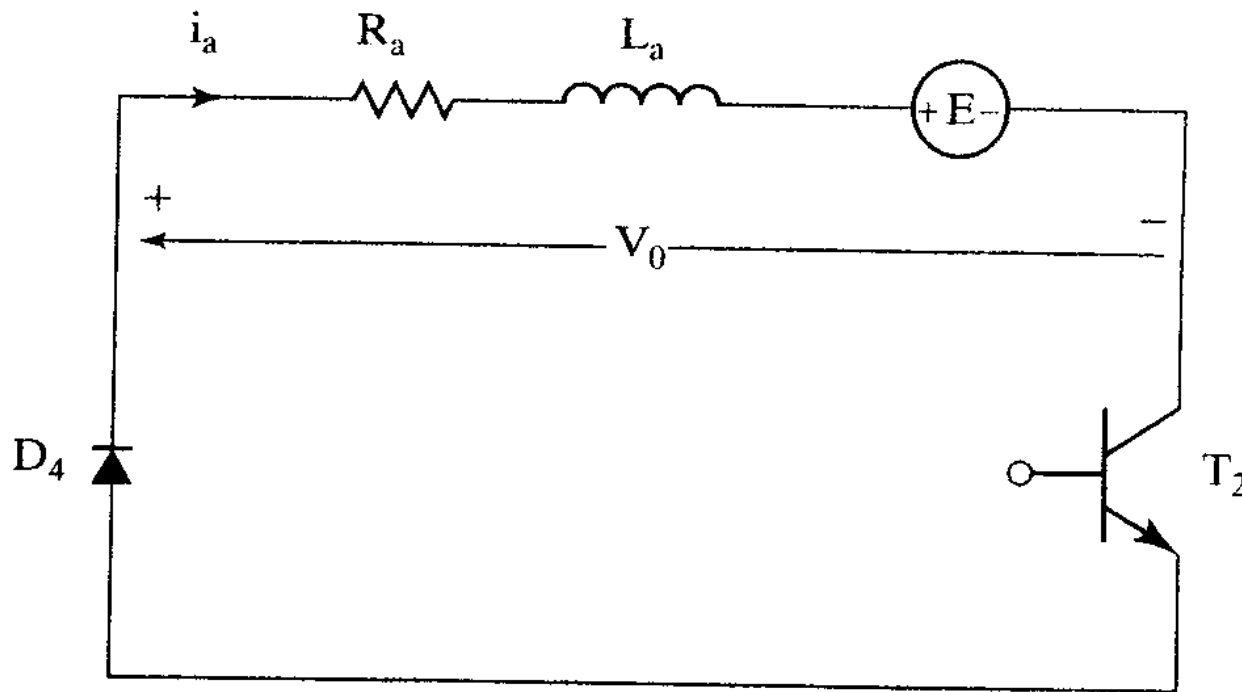


**Figure 4.4** First-quadrant operation with zero voltage across the load

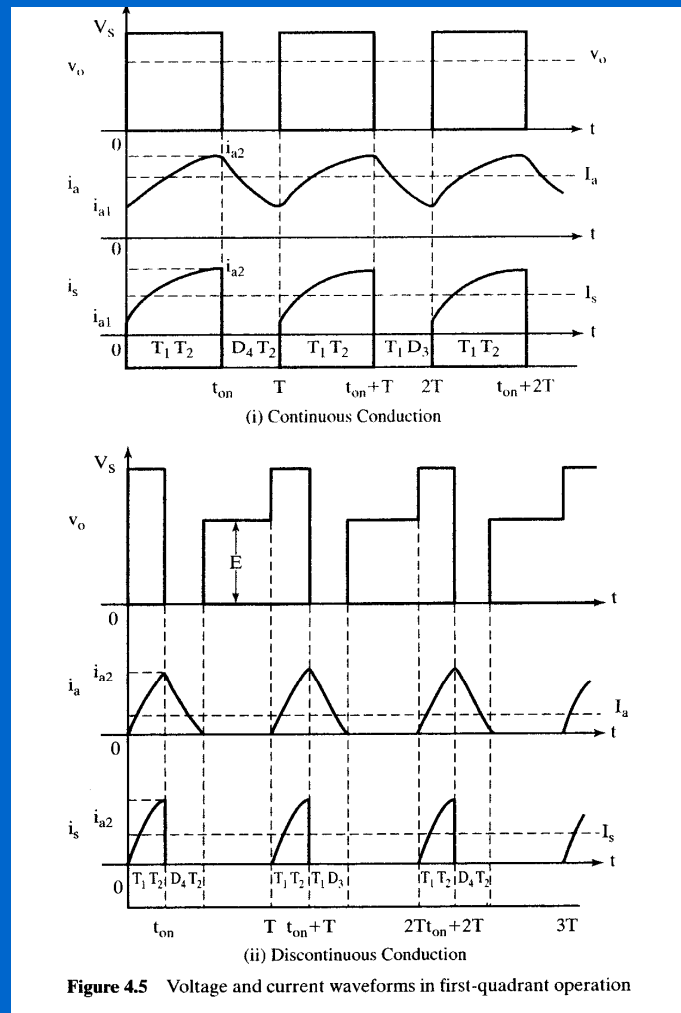- Fig. 4.5 voltage and current waveforms in first-quadrant operation.



- 
- 
- 
- Fig. 4.6 second-quadrant operation

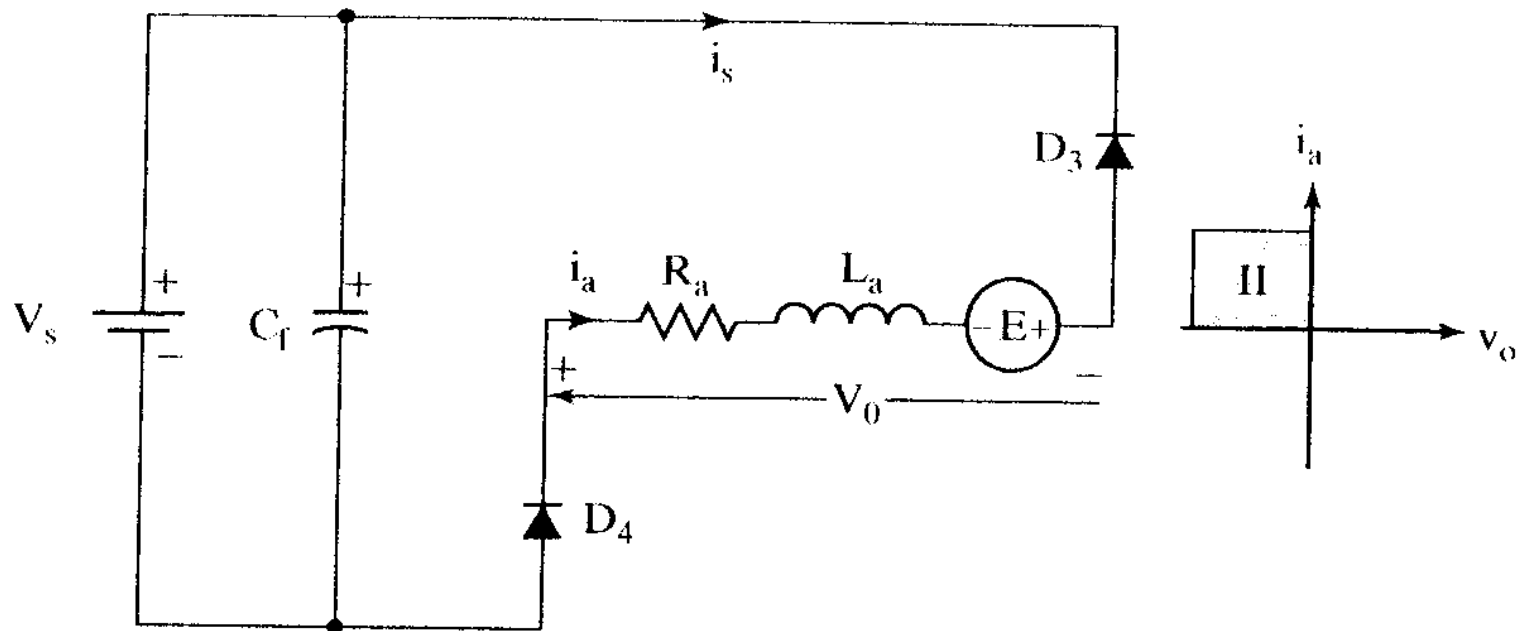

**Figure 4.6** Second-quadrant operation, with negative load voltage and positive current



- 
- 
- 
- Fig. 4.7 voltage and current waveforms in second-quadrant operation.


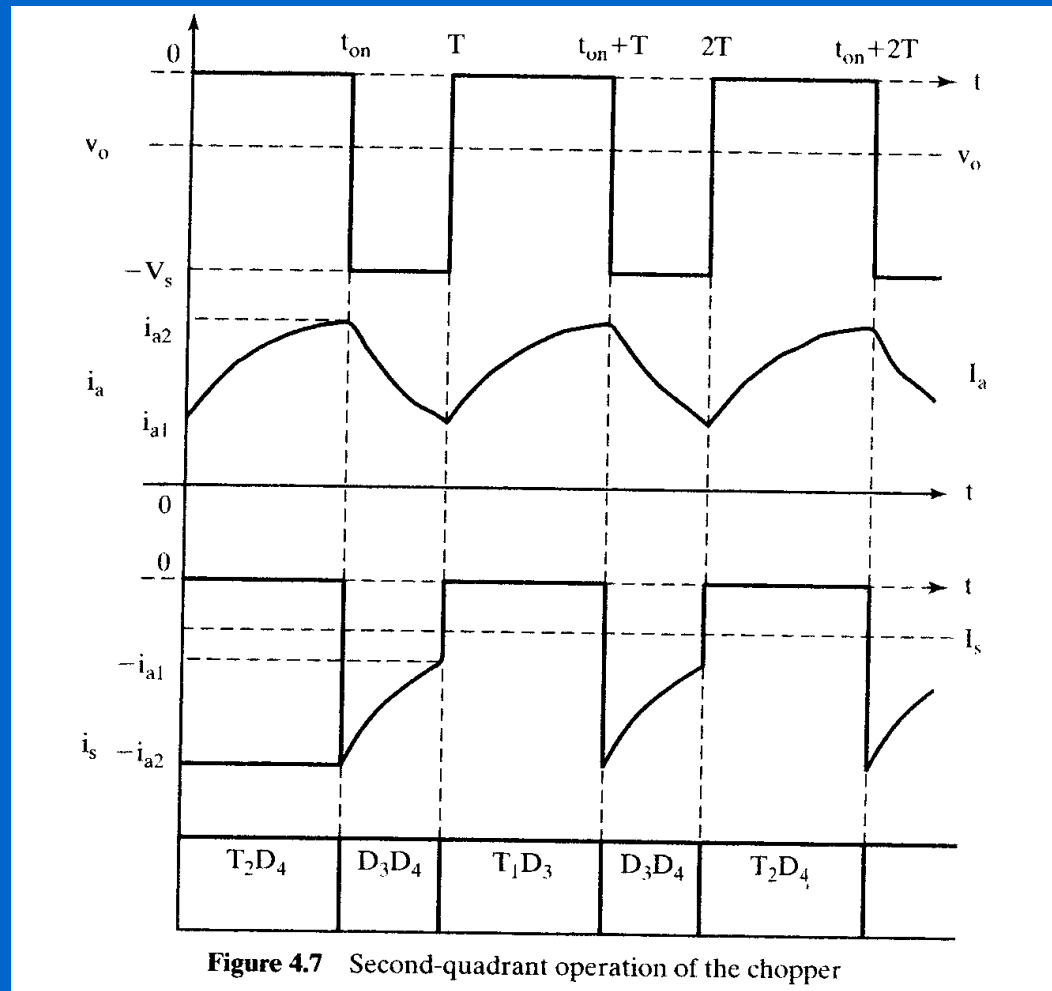



Figure 4.7 Second-quadrant operation of the chopper

- 
- 
- 
- Fig. 4.8 Modes of operation in the third quadrant.

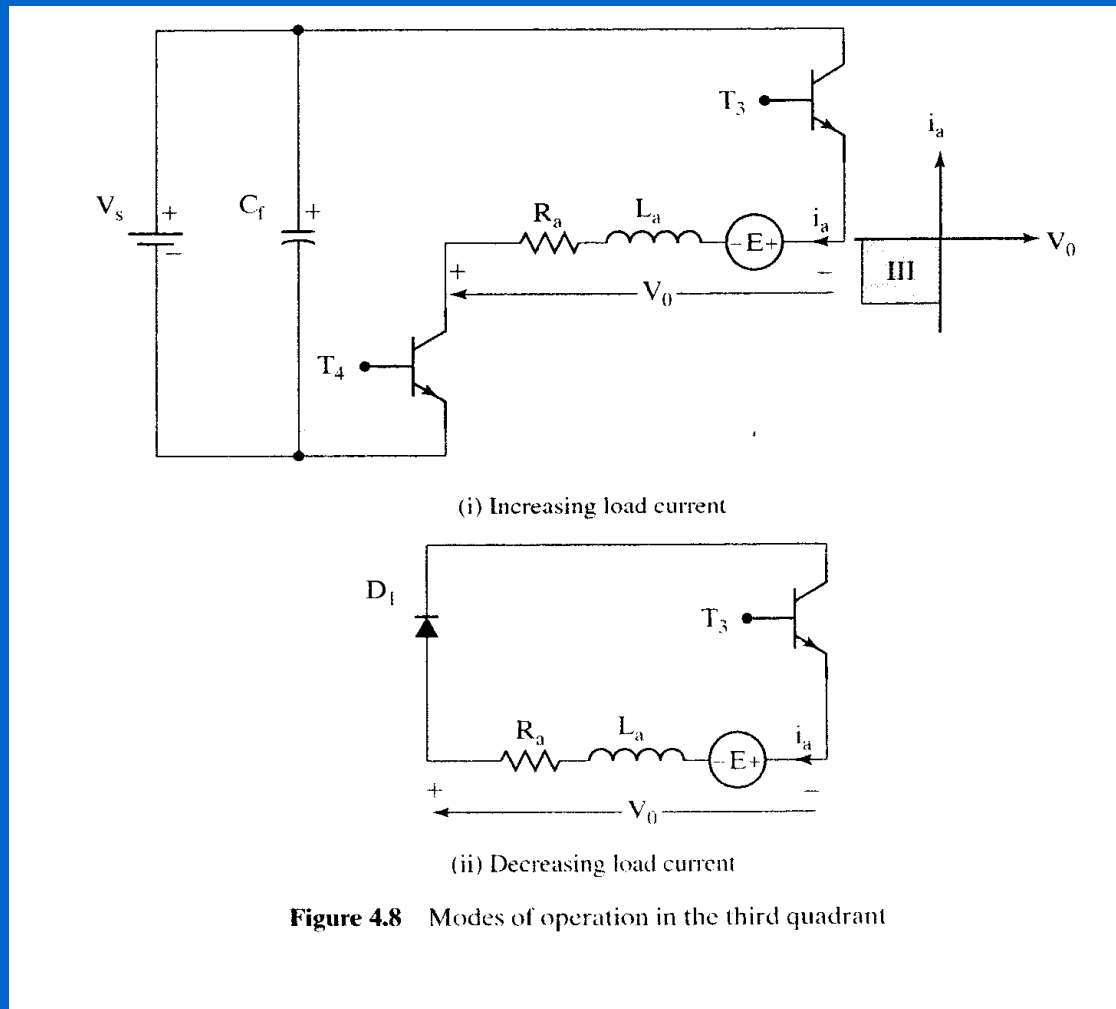

**Figure 4.8** Modes of operation in the third quadrant

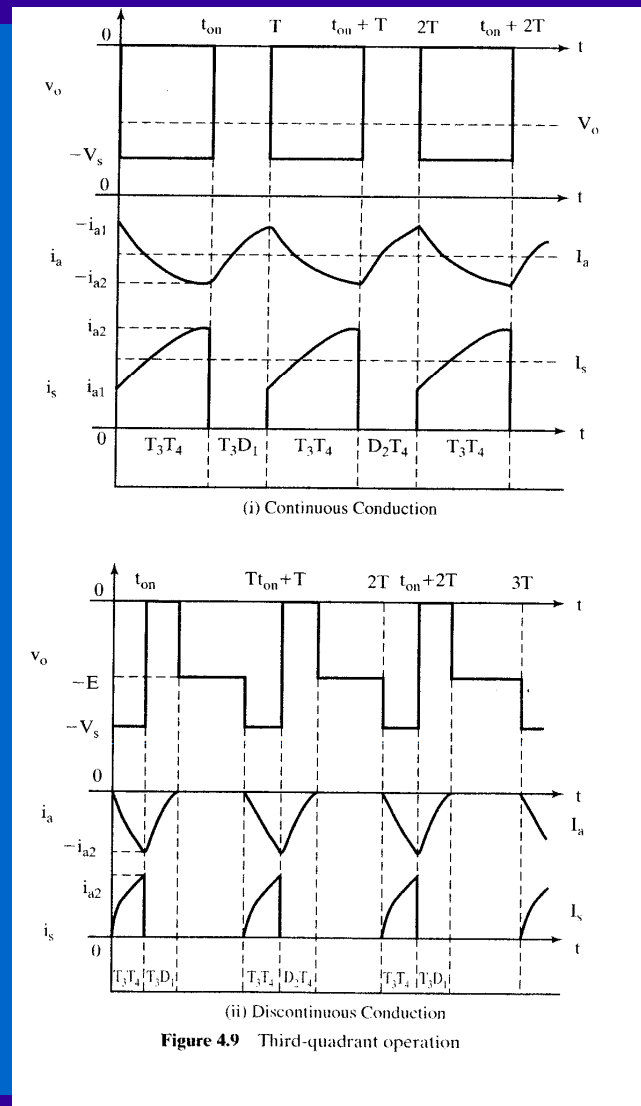- Fig. 4.9 waveform in third-quadrant operation



- Fig. 4.10 Waveforms in fourth-quadrant operation.

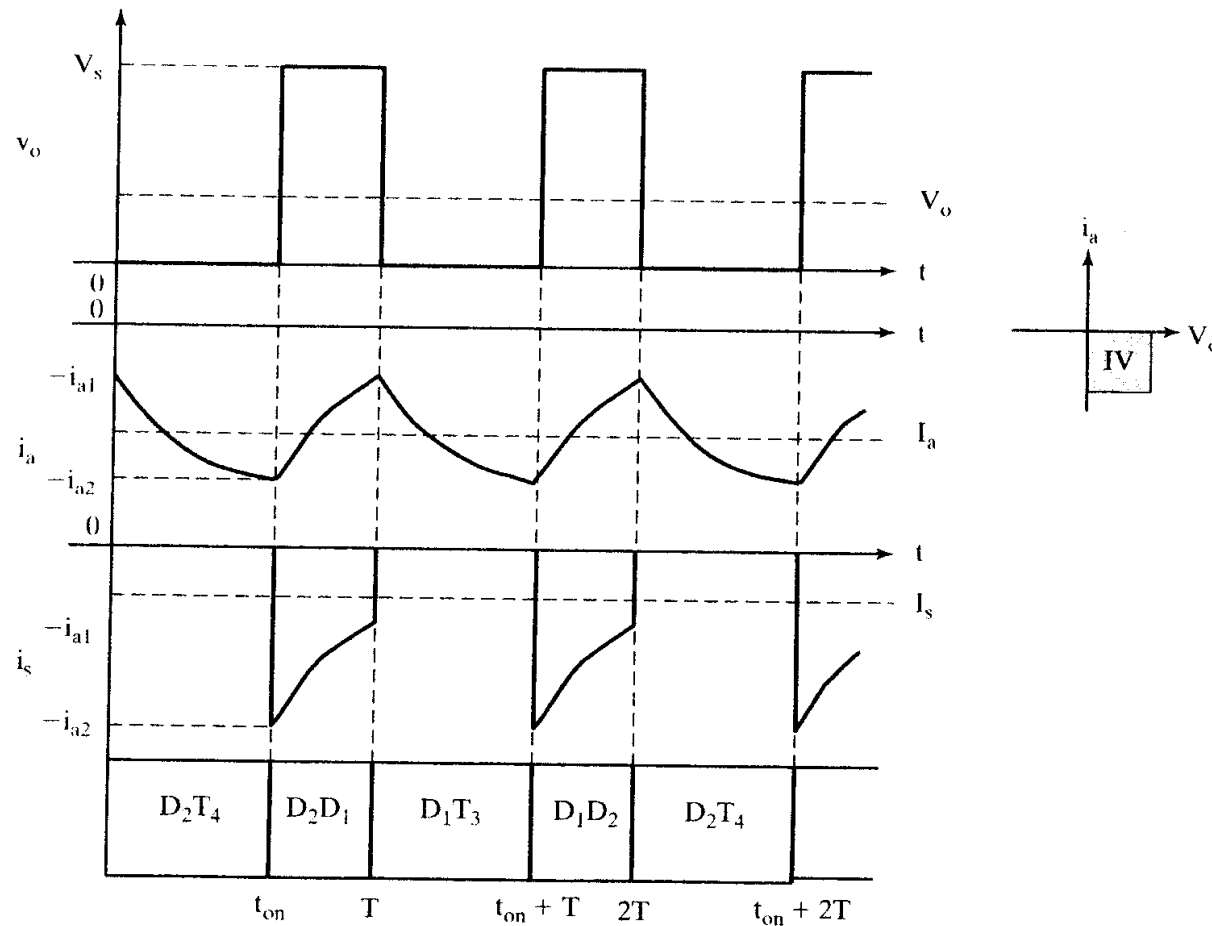


Figure 4.10 Fourth-quadrant operation of the chopper

•  
•  
•

## 4.4 Chopper for inversion

- Converter:  $DC \Rightarrow DC$  (different voltage)
- The chopper is the building block for that:  
 $AC \Rightarrow DC \Rightarrow DC$ (different voltage)

- 
- 
- 

## 4.5 Chopper with other power devices

- MOSFETs, IGBTs, GTOs, or SCRs are used for different power level.
- The MOSFET and transistor choppers are used at power levels up to 50kW.

- 
- 
- 

## 4.6 Model of The Chopper

- The transfer function of the chopper is

$$G_r(s) = \frac{K_r}{1 + \frac{sT}{2}}$$

where  $K_r = V_s/V_{cm}$ ,  $V_s$  is the source voltage, and  $V_{cm}$  is the maximum control voltage.

- Increasing the chopping frequency decreases the delay time, and its becomes a simple gain.

## 4.7 Input to the chopper

- The chopper input: a battery or a rectified ac supply.
- Fig. 4.11 is the chopper with rectified circuit.


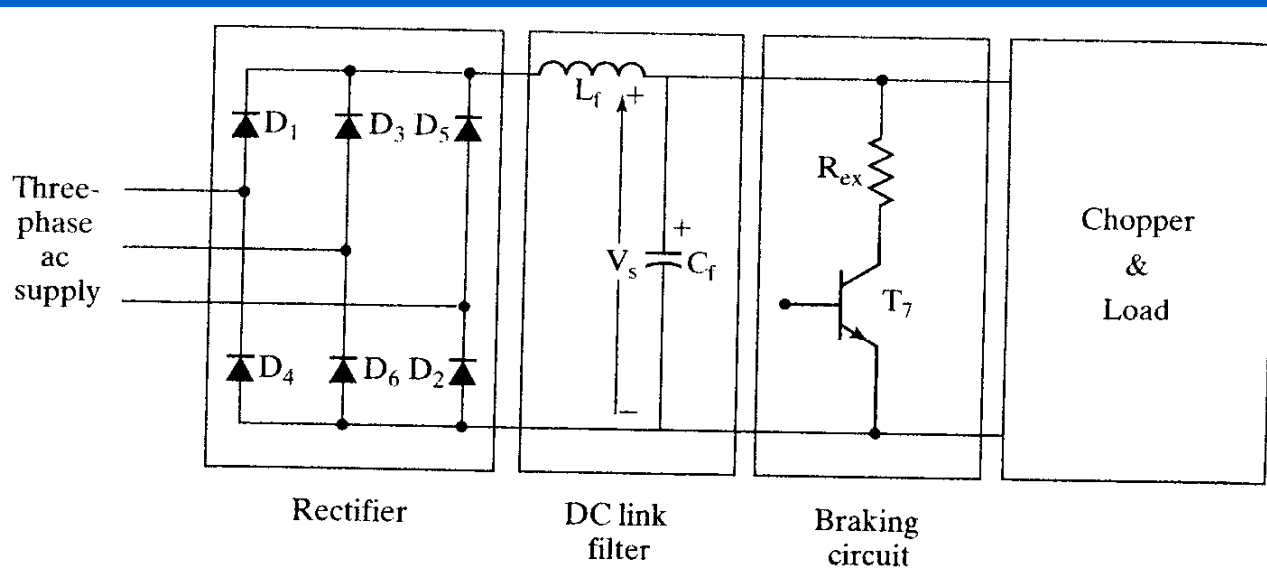


Figure 4.11 Front-end of the chopper circuit

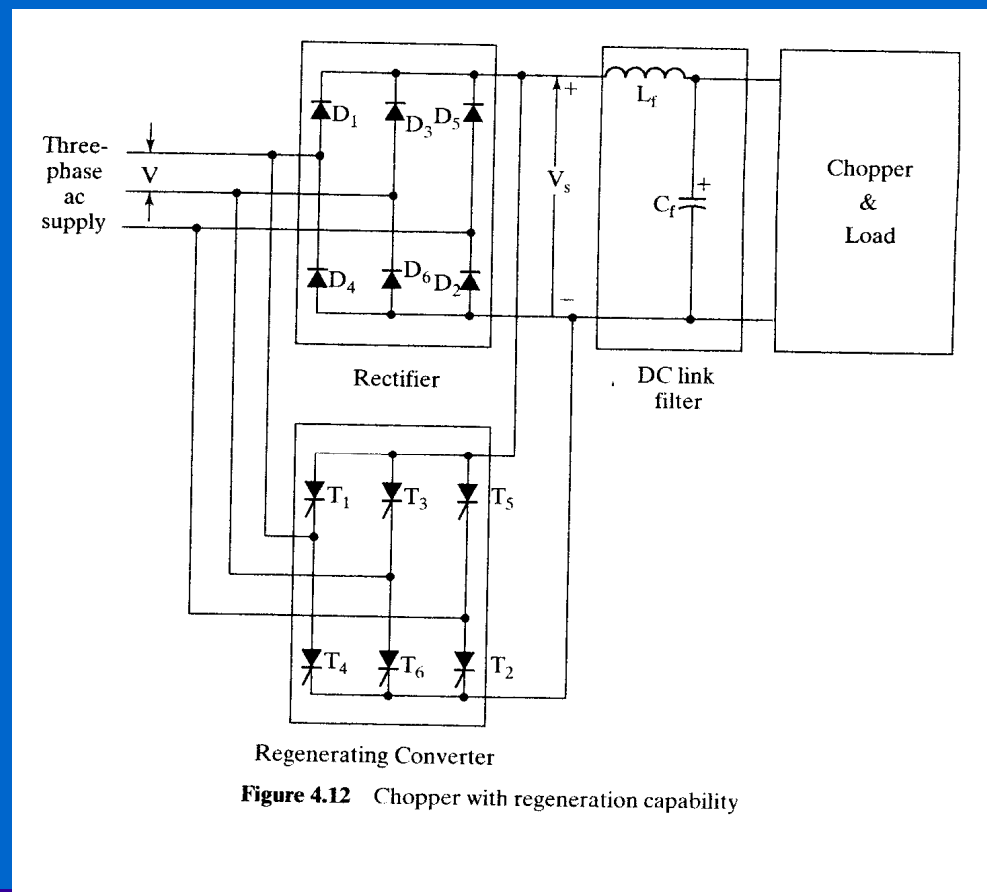

- Its disadvantage: it cannot transfer power from dc link into ac mains.
- Fig. 4.12 Chopper with regeneration capability



- 
- 
- 

- The generating converter has to be operated at triggering angles greater than  $90^\circ$ .

## 4.8 Other Chopper Circuits

- Fig. 4.13 one- and two-quadrant operation.

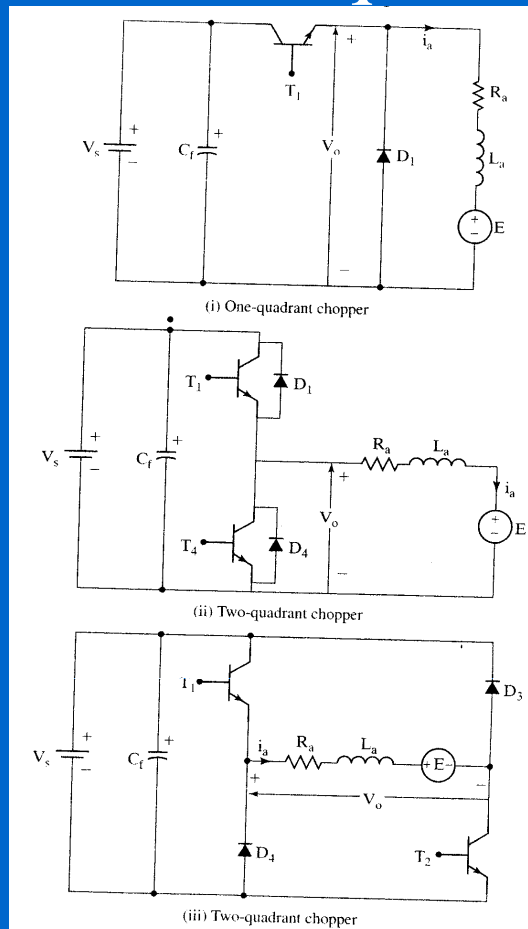


Figure 4.13 Variations of Figure 4.2 for one- and two-quadrant operation

•  
•  
•

## 4.9 Steady-state analysis ...

- 4.9.1 Analysis by averaging
- The average armature current is

$$I_{av} = \frac{V_{dc} - E}{R_a}$$

where  $V_{dc} = dV_s$

- The electromagnetic torque is

$$T_{av} = K_b I_{av} = K_b (dV_s - K_b \omega_m) / R_a \text{ (N}\cdot\text{m)}$$

- The normalized torque is

$$T_{\text{en}} = \frac{T_{\text{av}} / V_b}{T_b / V_b} = \frac{K_b(dV_s - K_b\omega_m) / V_b}{K_b I_b R_a / V_b} = \frac{dV_n - \omega_{mn}}{R_{\text{an}}}, \text{ p.u.}$$


where  $R_{\text{an}} = \frac{I_b R_a}{V_b}, \text{ p.u.}$      $V_n = \frac{V_s}{V_b}, \text{ p.u.}$      $\omega_{mn} = \frac{\omega_m}{\omega_b}, \text{ p.u.}$

- 4.9.2 Instantaneous steady-state computation (including harmonics)
- The equations of the motor for on and off times (continuous current conduction)


$$V_s = E + R_a i_a + L_a \frac{di_a}{dt}, \quad 0 \leq t \leq dT$$

$$0 = E + R_a i_a + L_a \frac{di_a}{dt}, \quad dT \leq t \leq T$$

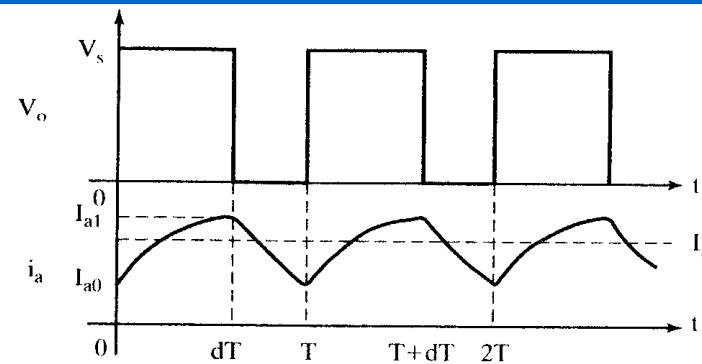- 
- 
- 
- Fig. 4.15 The waveform of applied voltage and armature current.



(i) Continuous Conduction

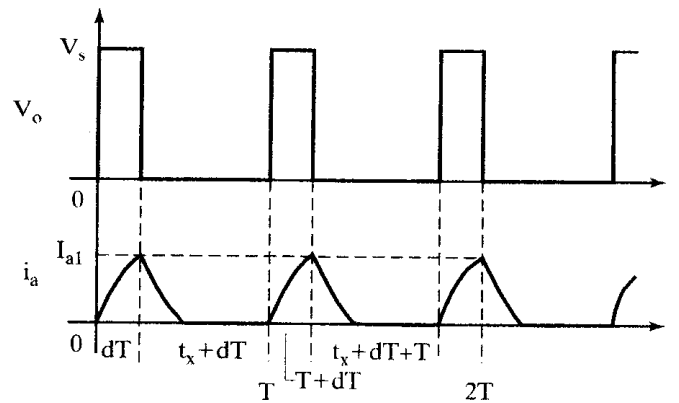

(ii) Discontinuous Conduction

**Figure 4.15** Applied voltage and armature current in a chopper-controlled dc motor drive

- 
- 
- 
- The solutions of the above equations:

$$i_a(t) = \frac{V_s - E}{R_a} (1 - e^{-\frac{t}{T_a}}) + I_{a0} e^{-\frac{t}{T_a}}, \quad 0 < t < dT$$

$$i_a(t) = -\frac{E}{R_a} (1 - e^{-\frac{t^1}{T_a}}) + I_{a1} e^{-\frac{t^1}{T_a}}, \quad dT \leq t \leq dT$$

where  $T_a = L_a/R_a$  (Armature time constant)

$$t^1 = t - dT$$

- By using boundary condition

$$I_{a1} = \frac{V_s(1 - e^{-dT/T_a})}{R_a(1 - e^{-T/T_a})} - \frac{E}{R_a} \quad I_{a0} = \frac{V_s(e^{dT/T_a} - 1)}{R_a(e^{T/T_a} - 1)} - \frac{E}{R_a}$$

- 
- 
- 

- The critical duty cycle: the limiting or minimum value of duty cycle for continuous current;  $I_{a0}$  equates to zero.
- The relevant equations for discontinuous current-conduction mode

$$V_s = E + R_a i_a + L_a \frac{di_a}{dt}, \quad 0 \leq t \leq dT$$

$$0 = E + R_a i_a + L_a \frac{di_a}{dt}, \quad dT \leq t \leq t_x + dT$$

$$\text{with } i_a(t_x + dT) = 0; \quad i_a(0) = 0$$



- 
- 
- 
- Hence,

$$I_{a1} = \frac{V_s - E}{R_a} (1 - e^{-dT/T_a})$$

$$i_a(t_x + dT) = -\frac{E}{R_a} (1 - e^{-\frac{t_x}{T_a}}) + I_{a1} e^{-\frac{t_x}{T_a}}$$

- $t_x$  is evaluated from (4.25) and the above eqs. as

$$t_x = T_a \log_e \left[ 1 + \frac{I_{a1} R_a}{E} \right]$$

- 
- 
- 

- The solution for the armature current in three time segments is

$$i_a(t) = \frac{V_s - E}{R_a} (1 - e^{-\frac{t}{T_a}}), \quad 0 < t < dT$$

$$i_a(t) = I_{a1} e^{-\frac{(t-dT)}{T_a}} - \frac{E}{R_a} (1 - e^{-\frac{(t-dT)}{T_a}}), \quad dT \leq t \leq t_x - dT$$

$$i_a(t) = 0, \quad (t_x + dT) < t < T$$

•  
•  
•

## 4.10 Rating of the device


- The rms value of the power switch current

$$I_t = \sqrt{\frac{I_{\max}^2}{2T} (T + dT)} = \sqrt{\frac{1+d}{2}} \cdot I_{\max}$$

- The average diode current

$$I_d = \left(\frac{1-d}{2}\right) \cdot I_{\max}$$

- Transistor and diode currents for motoring operation in the continuous-conduction mode.

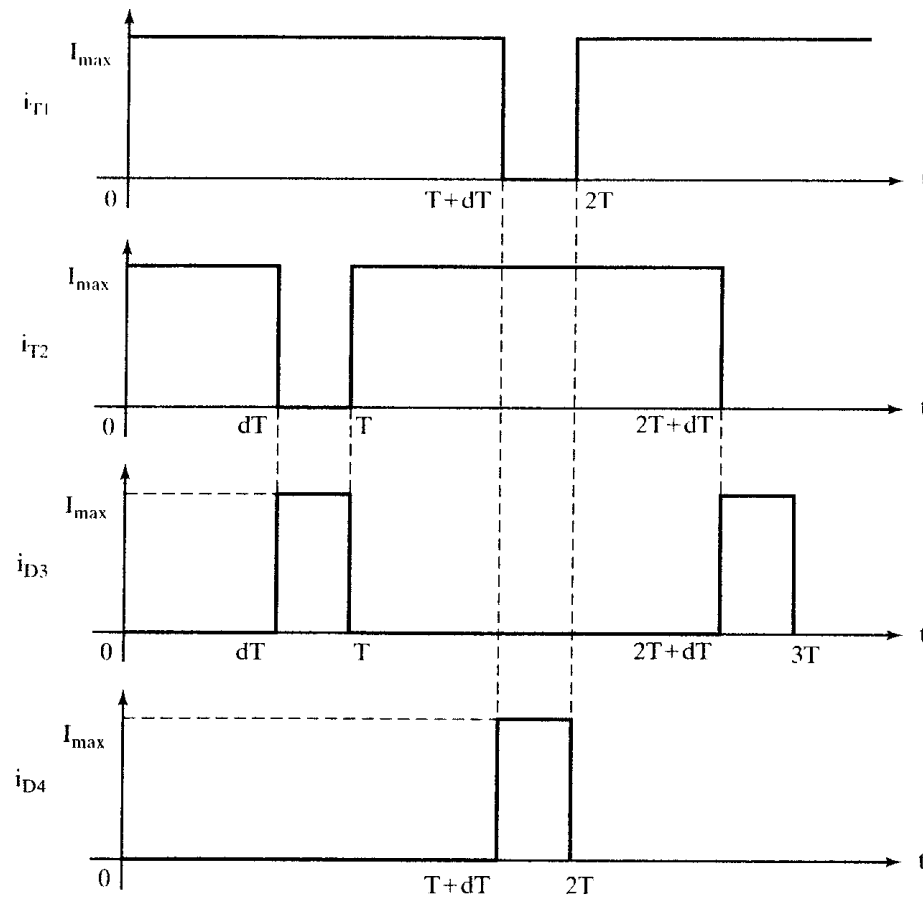

**Figure 4.17** Transistor and diode currents in the chopper for motoring operation in the continuous-conduction mode

•  
•  
•

## 4.11 Pulsating Torque

- The average of the harmonic torque is zero.
- High-performance applications require the pulsating torque to be minimum.
- The applied voltage is resolved into Fourier components as

$$V_a(t) = V_a + \sum_{n=1}^{\infty} A_n \sin(n\omega_c t + \theta_n)$$

where  $V_a = \frac{dT}{T} V_s = dV_s$        $\omega_c = 2\pi f_c = \frac{2\pi}{T}$

$$A_n = \frac{2V_s}{n\pi} \sin \frac{n\omega_c dT}{2} \quad \theta_n = \frac{\pi}{2} - \frac{n\omega_c dT}{2}$$

• • • • • • • • •

- 
- 
- 
- The armature current is expressed as

$$i_a(t) = I_{av} + \sum_{n=1}^{\infty} \frac{A_n}{|Z_n|} \sin(n\omega_c t + \theta_n - \phi_n)$$

where  $I_{av} = \frac{V_a - E}{R_a}$      $Z_n = R_a + jn\omega_c L_a$

$$\phi_n = \cos^{-1} \left\{ \frac{R_a}{\sqrt{R_a^2 + n^2 \omega_c^2 L_a^2}} \right\}$$

- The input power is

$$P_i = V_a(t) i_a(t)$$

$$= \left\{ \begin{array}{l} V_a I_{av} + I_{av} \sum_{n=1}^{\infty} A_n \sin(n\omega_c t + \theta_n) \\ + V_a \sum_{n=1}^{\infty} \frac{A_n}{|Z_n|} \sin(n\omega_c t + \theta_n - \phi_n) + \sum_{n=1}^{\infty} \left( \frac{A_n^2}{|Z_n|} \sin(n\omega_c t + \theta_n) \sin(n\omega_c t + \theta_n - \phi_n) \right) \end{array} \right\}$$

## 4.12 Closed-loop operation

- Fig. 4.20 is the closed-loop speed-controller dc motor drive.


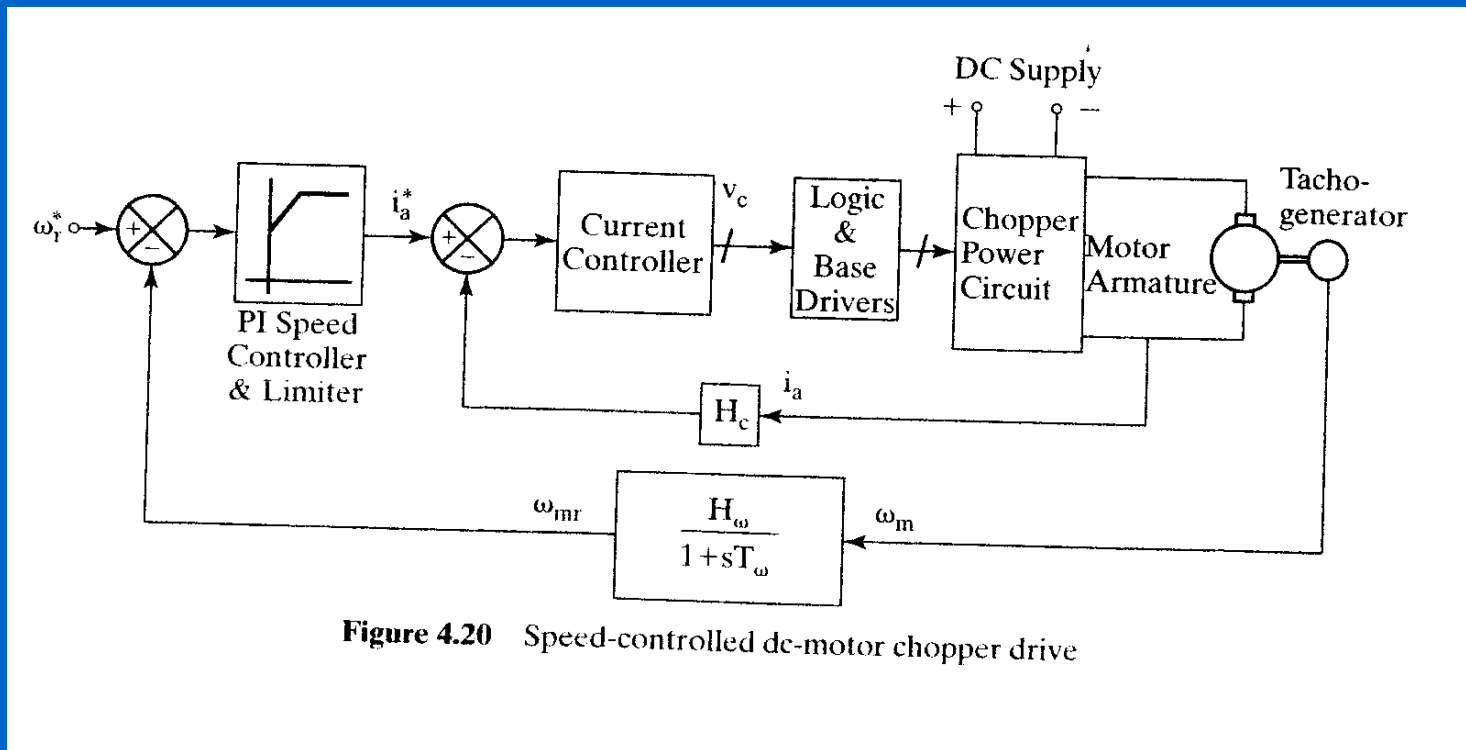


Figure 4.20 Speed-controlled dc-motor chopper drive

- 
- 
- 
- The current controller can be
  - Pulse-Width-Modulation (PWM) controller
  - Hysteresis controller


Fig. 4.21 shows on- and off-time for PWM

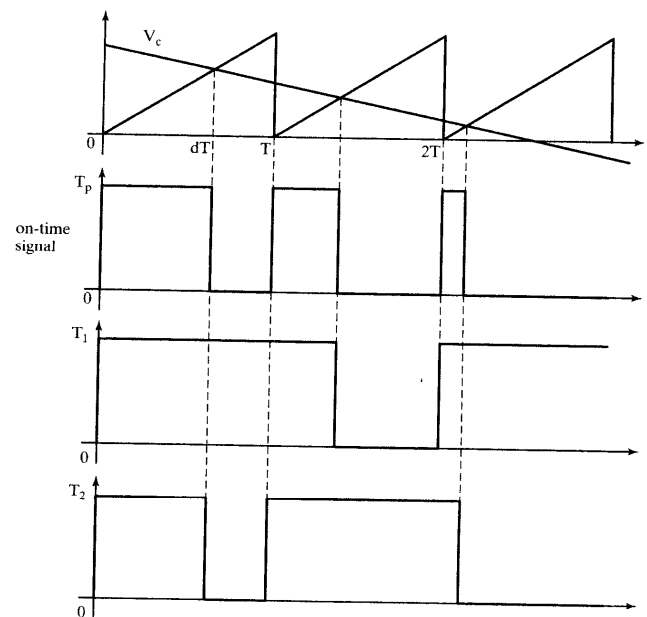

**Figure 4.21** Generation of base-drive signals from current error for forward motoring when one is using the chopper shown in Figure 4.2



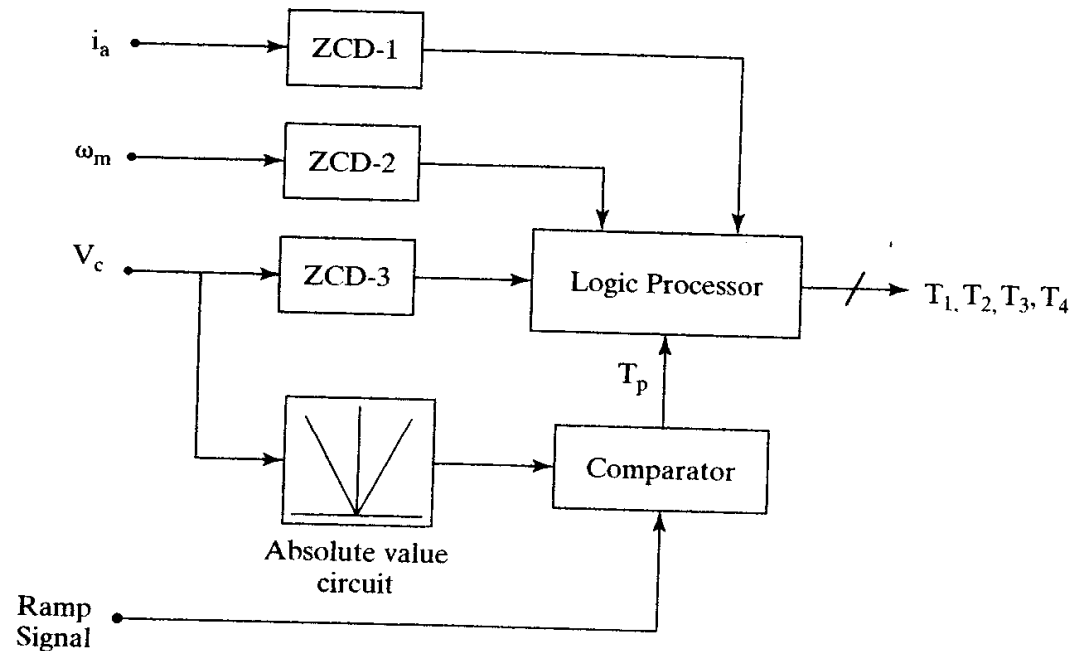- Fig. 4.22 is the implementation of PWM current controller.




Note : ZCD — Zero Crossing Detector for polarity detection

**Figure 4.22** PWM current-controller implementation with ramp carrier signal


- 
- 
- 
- Fig. 4.24 shows hysteresis-controlled operation

$$i_a \leq i_a^* - \Delta i, \quad \text{set } v_a = V_s$$

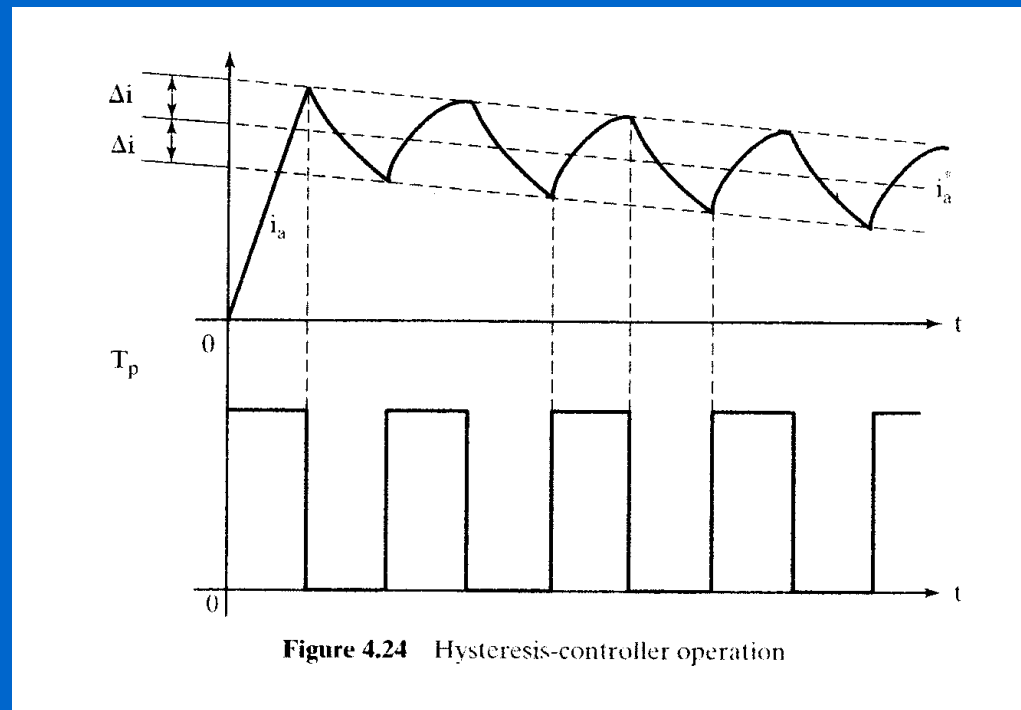
$$i_a \geq i_a^* + \Delta i, \quad \text{reset } v_a = 0$$



- 
- 
- 
- Fig. 4.23

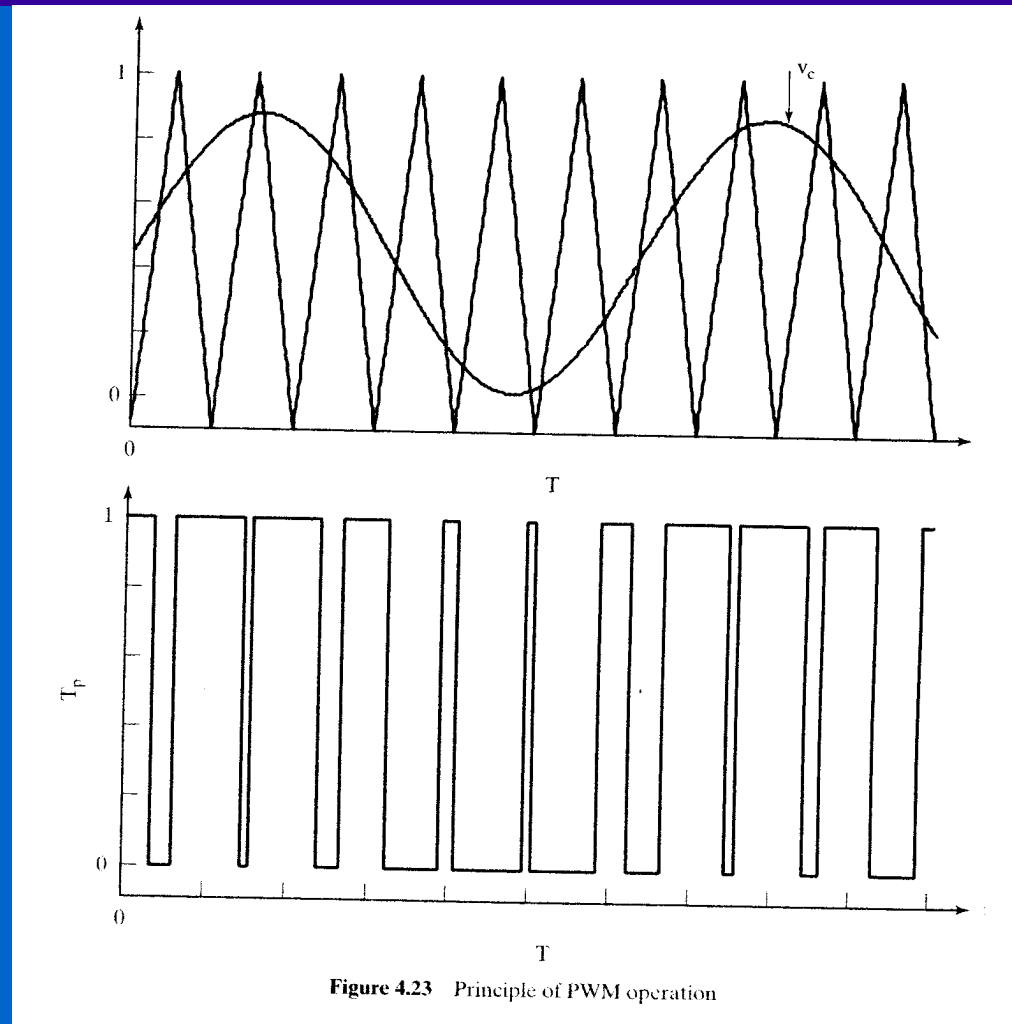

- 
- 
- 
- Fig. 4.25 is realization of hysteresis controller.

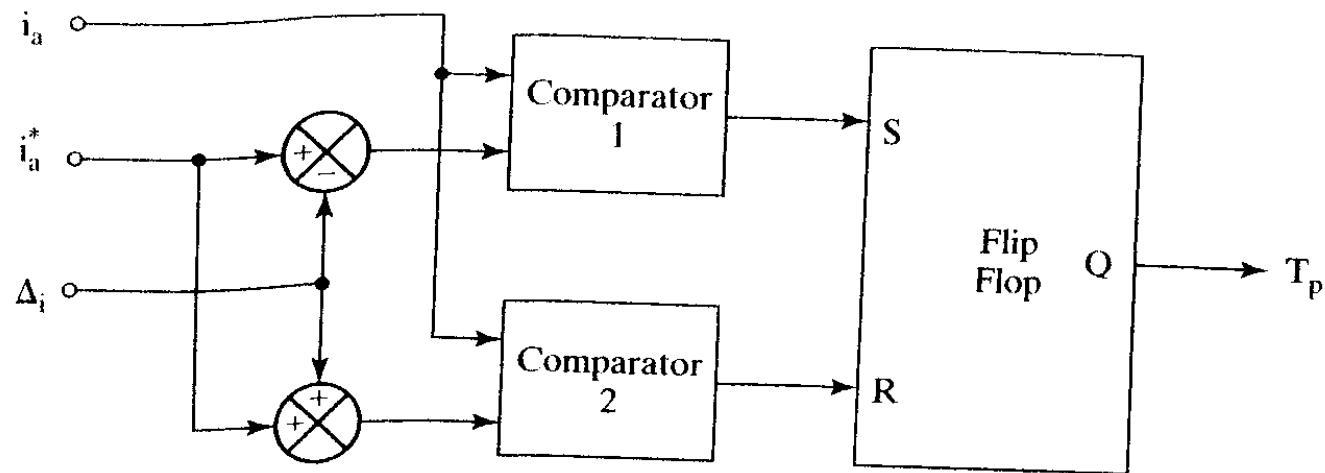

**Figure 4.25** Realization of hysteresis controller