

-
-
-

7 Frequency-controlled induction motor drives

- The relationship between the synchronous speed and the frequency

$$n_s = \frac{120f_s}{P}$$

- 7.2 Static frequency changes

- There are two types

direct: cycloconverters

indirect: a rectification and an inverter

-
-
-
- Cycloconverter drive

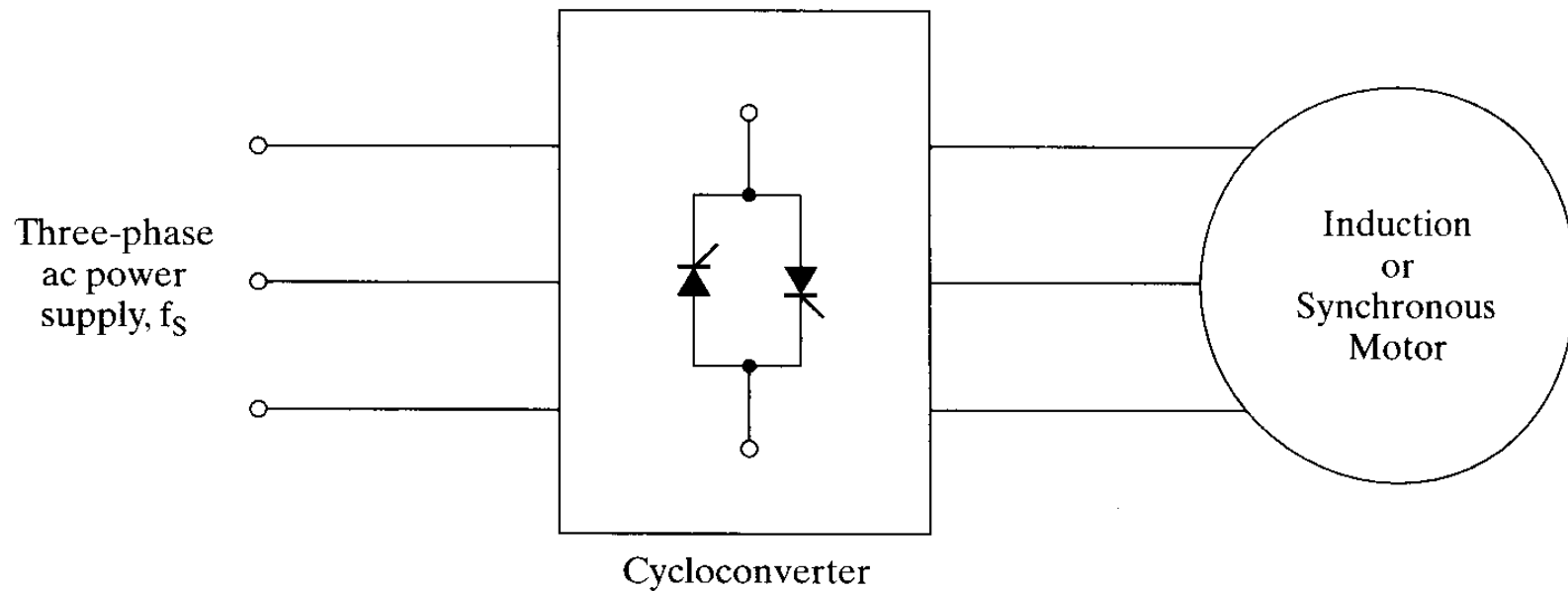


Figure 7.1 Cycloconverter-driven induction or synchronous motor drive

-
-
-
- PWM inverter

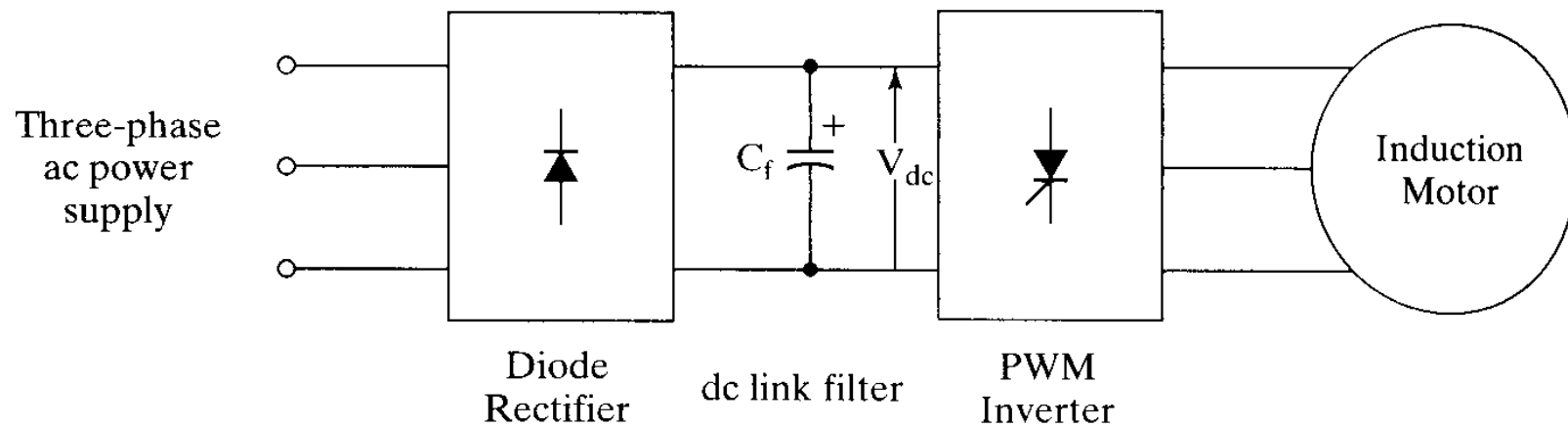


Figure 7.2 PWM inverter fed induction motor drive

-
-
-
- Direct (cycloconverter): The output frequency has a range of from 0 to $0.5f_s$. $0.33f_s$ for better waveform control.
- Indirect: broadly classified depending on the feeding source, voltage or current source
- Variable-voltage, variable-frequency drive

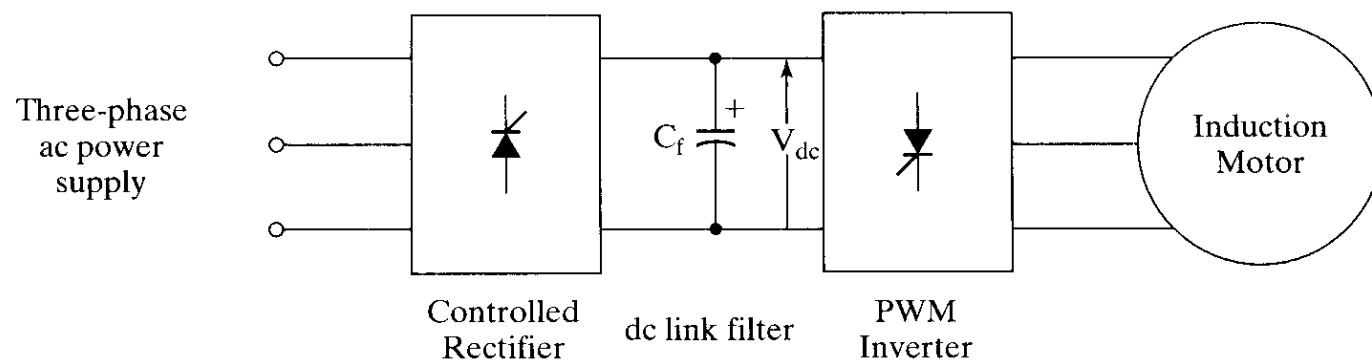


Figure 7.3 Variable-voltage, variable-frequency (VVVF) induction motor drive

- Regenerative voltage-source inverter-fed ac drive

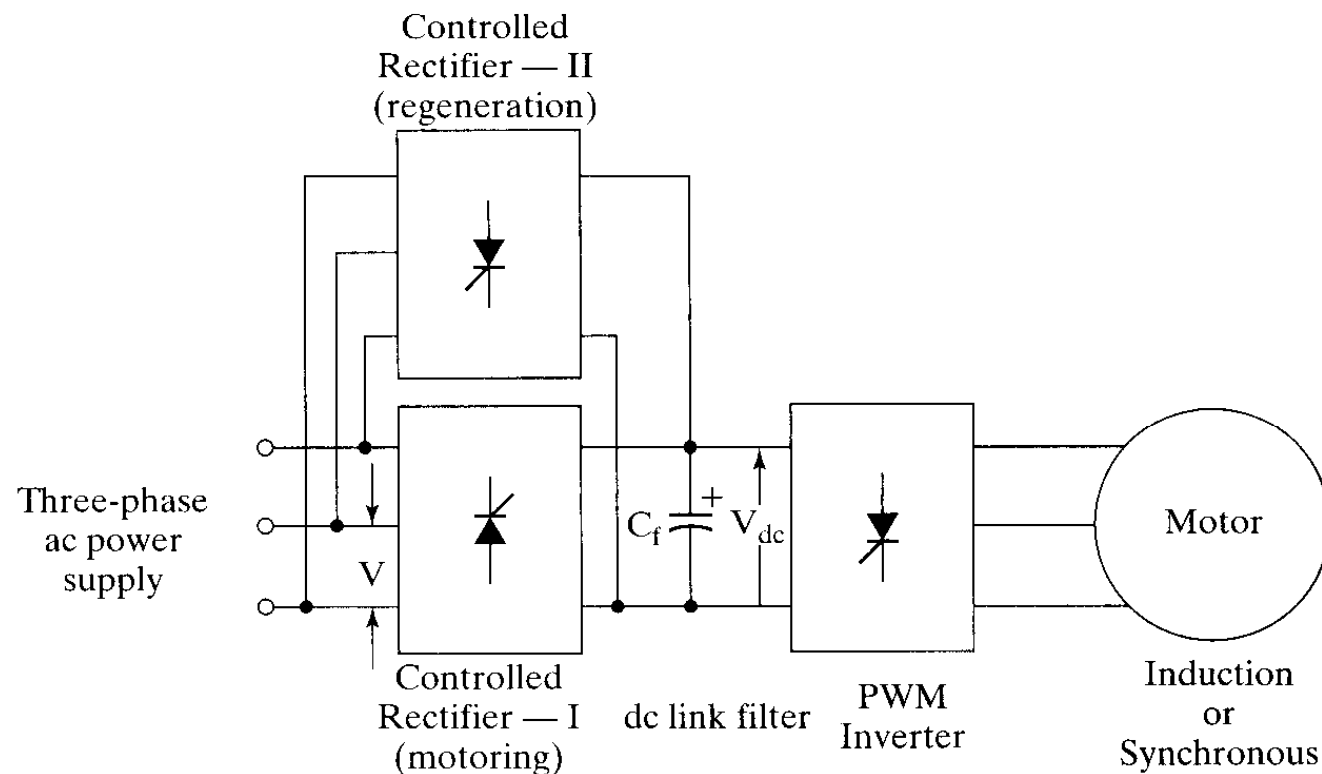


Figure 7.4 Regenerative voltage-source inverter-fed ac drive

- Current-regulated voltage-source-driven drive

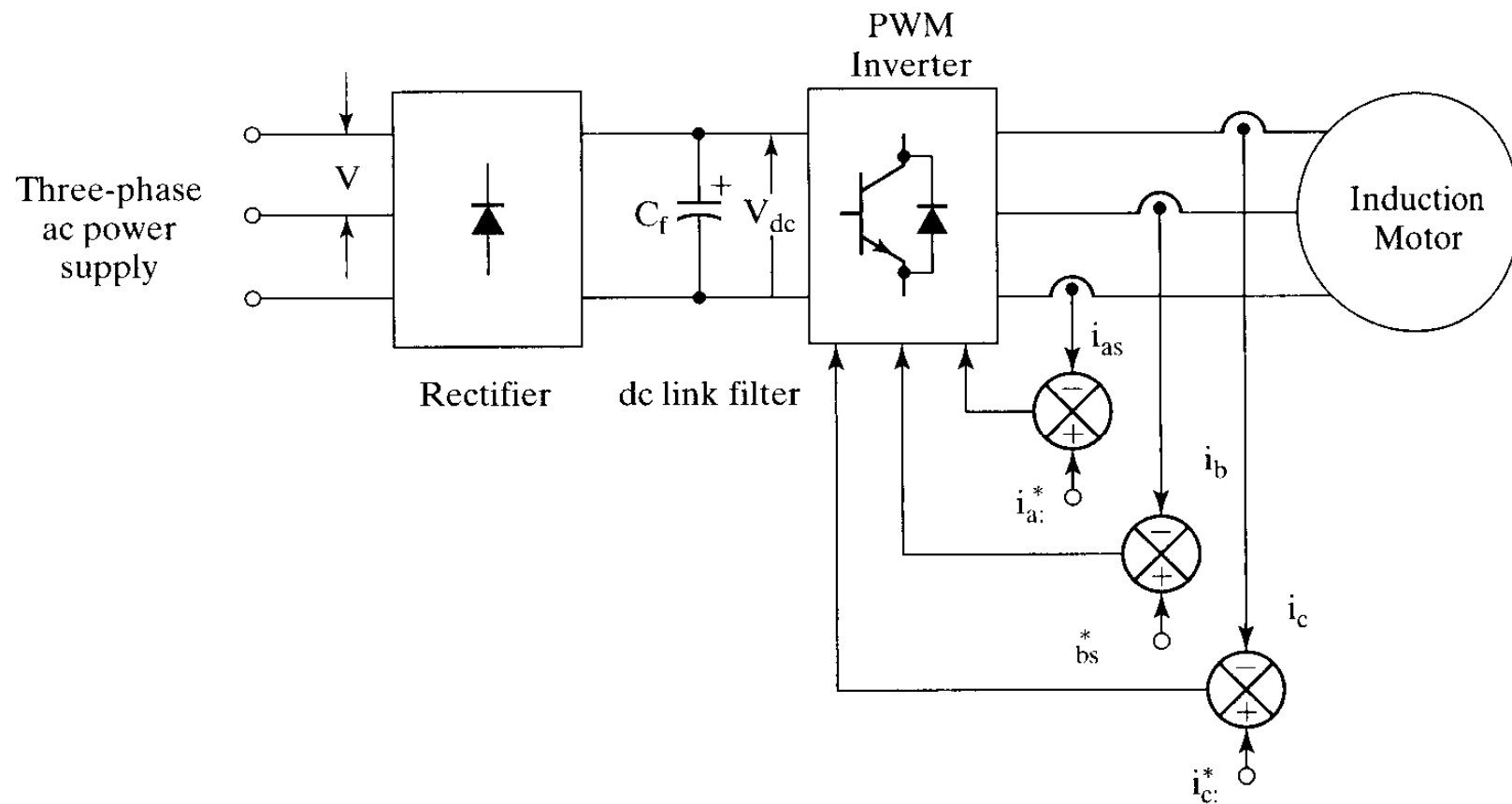


Figure 7.5 Current-regulated voltage-source-driven induction motor drive

-
-
-
- **Current-source inverter-driven drive**

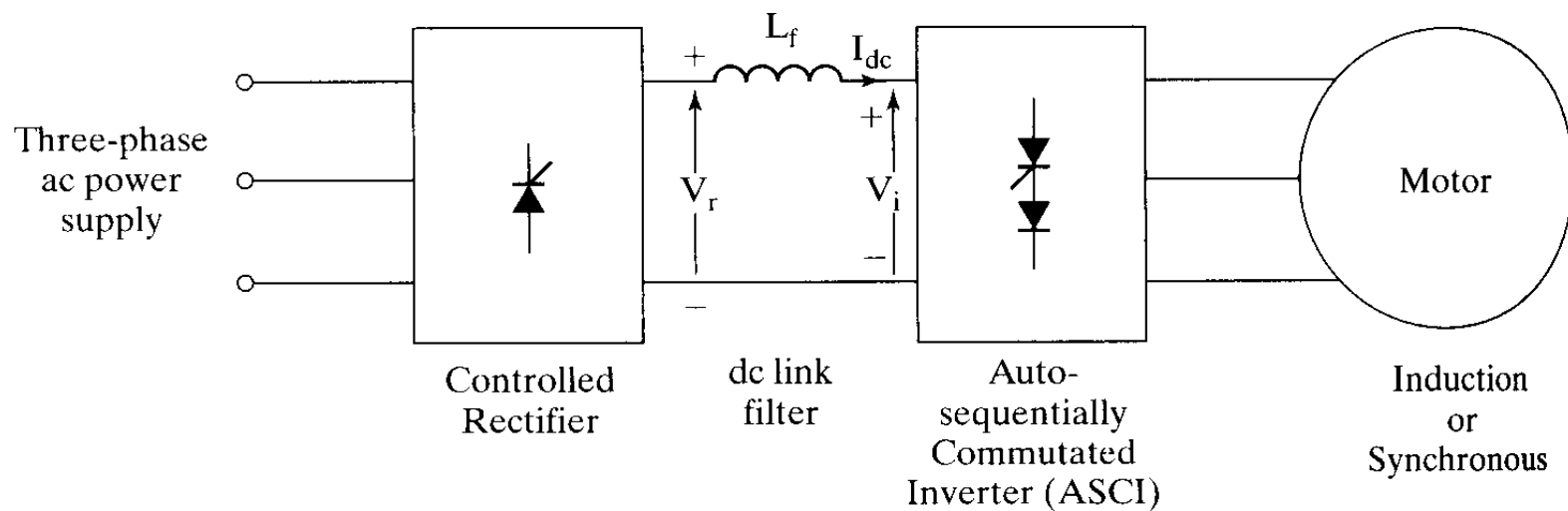


Figure 7.6 Current-source inverter-driven induction or synchronous motor drive

- Classification of frequency changer

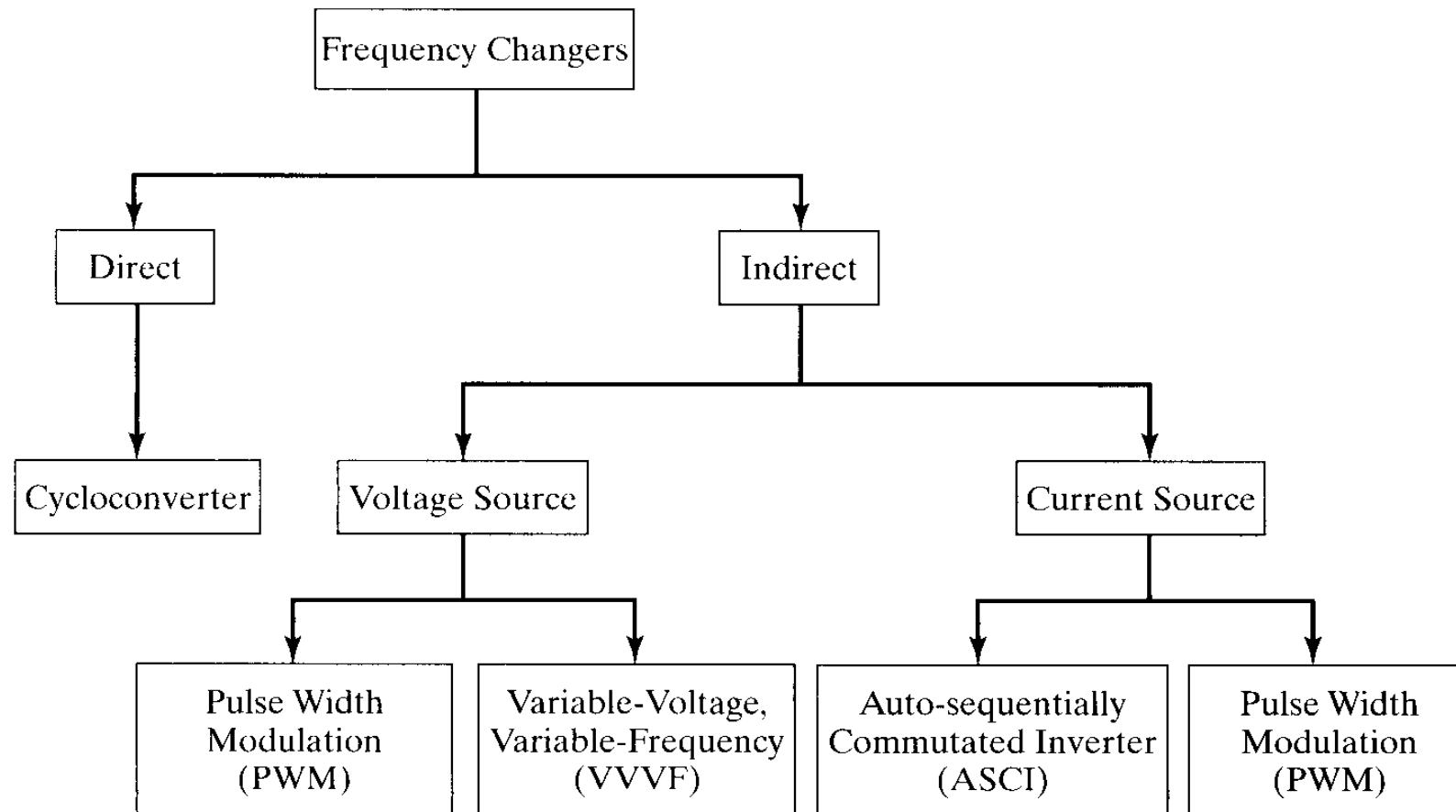


Figure 7.7 Classification of frequency changers

•
•
•

7.3 Voltage-source inverter

- A half-bridge modified McMurray inverter.

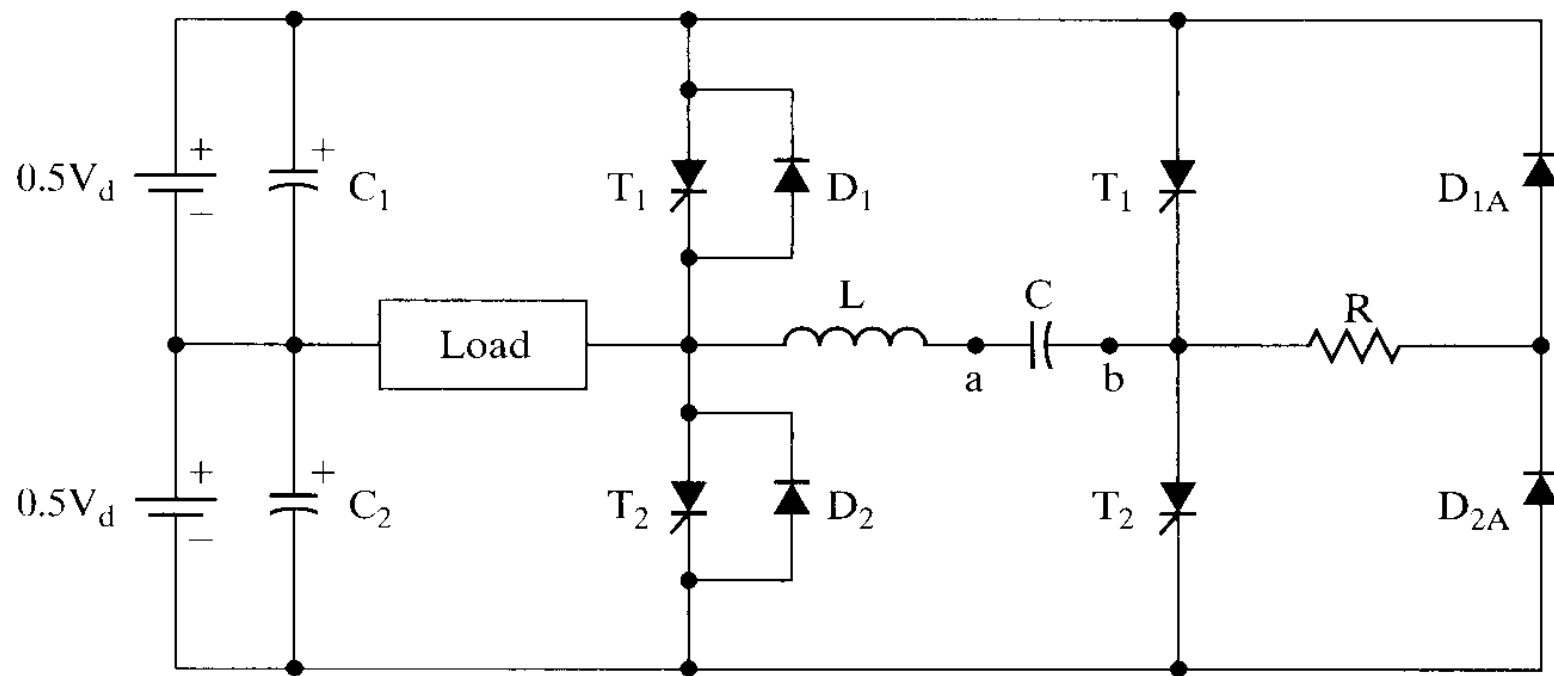


Figure 7.8 Half-bridge voltage-source inverter

-
-
-
- Snubbers: across transistors or SCR to limit dv/dt and its effects.
- (a) Half-bridge inverter charging

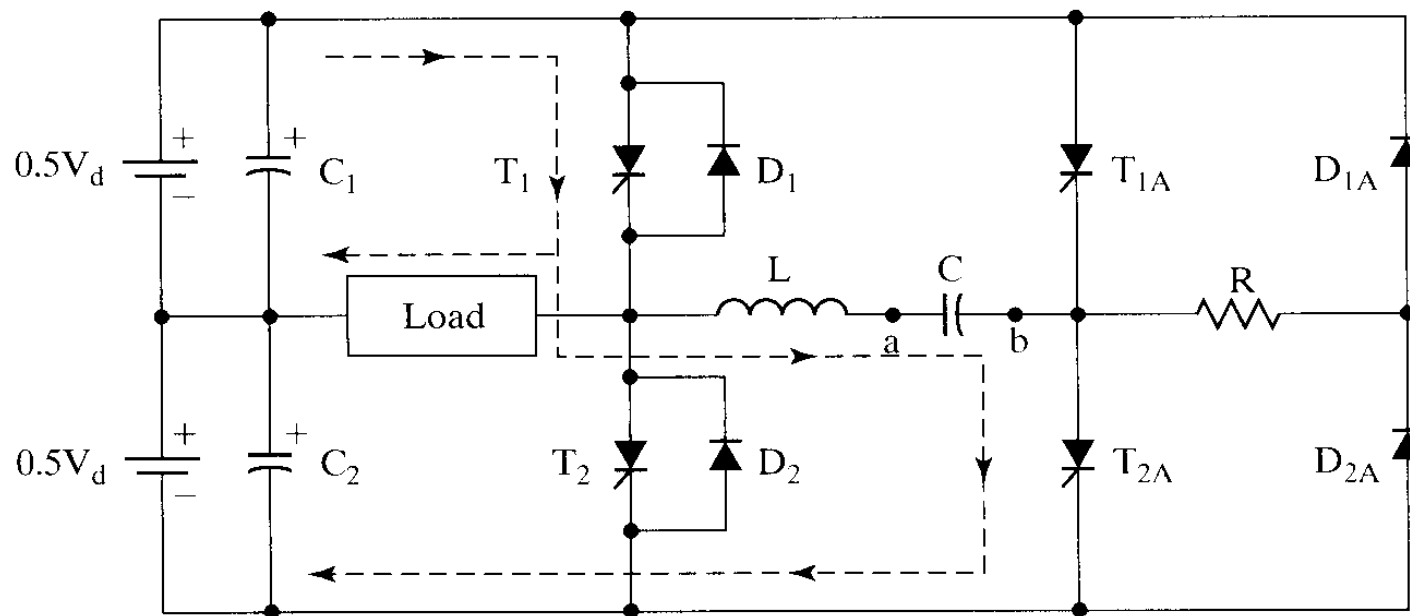


Figure 7.9a (a) Half-bridge voltage-source inverter charging

-
-
-
- (b) Half-bridge inverter communication

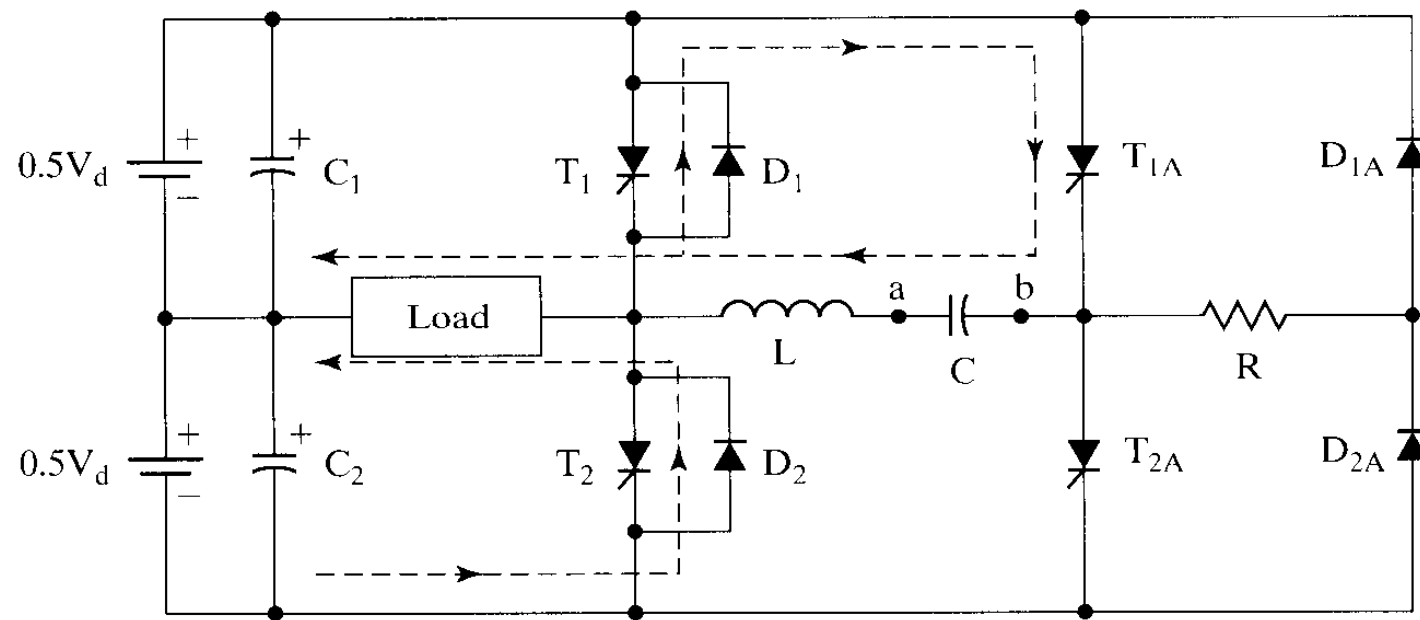


Figure 7.9b (b) Half-bridge voltage-source inverter commutation

- The frequency of the load voltage is determined by the rate at which T_1 and T_2 are enabled.
- A full-bridge inverter

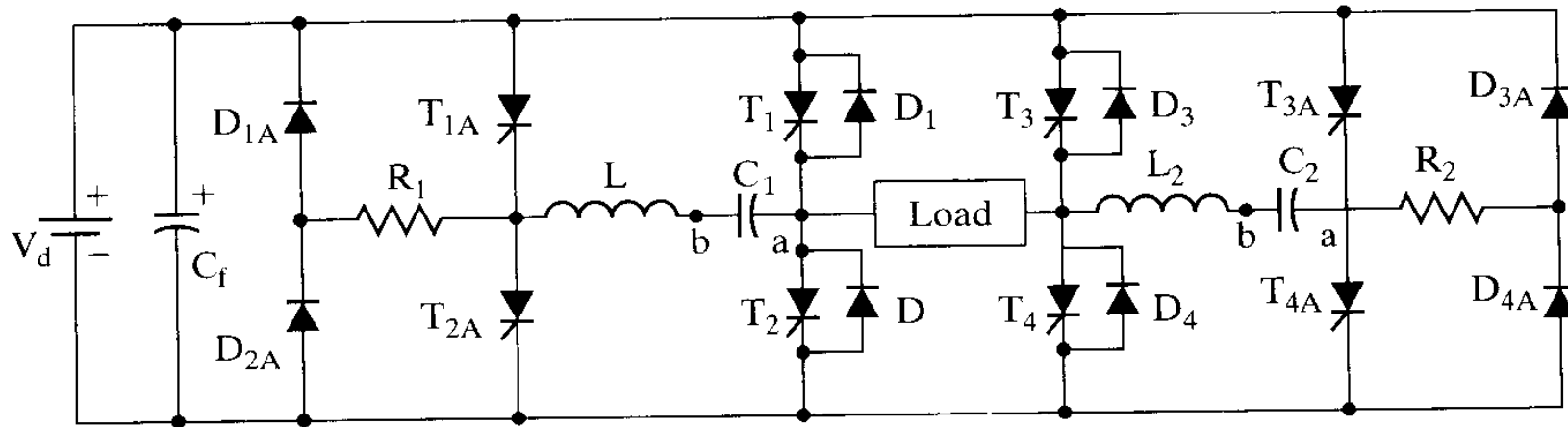


Figure 7.10 Full-bridge voltage-source inverter

-
-
-
- Voltage-source inverter with transistors

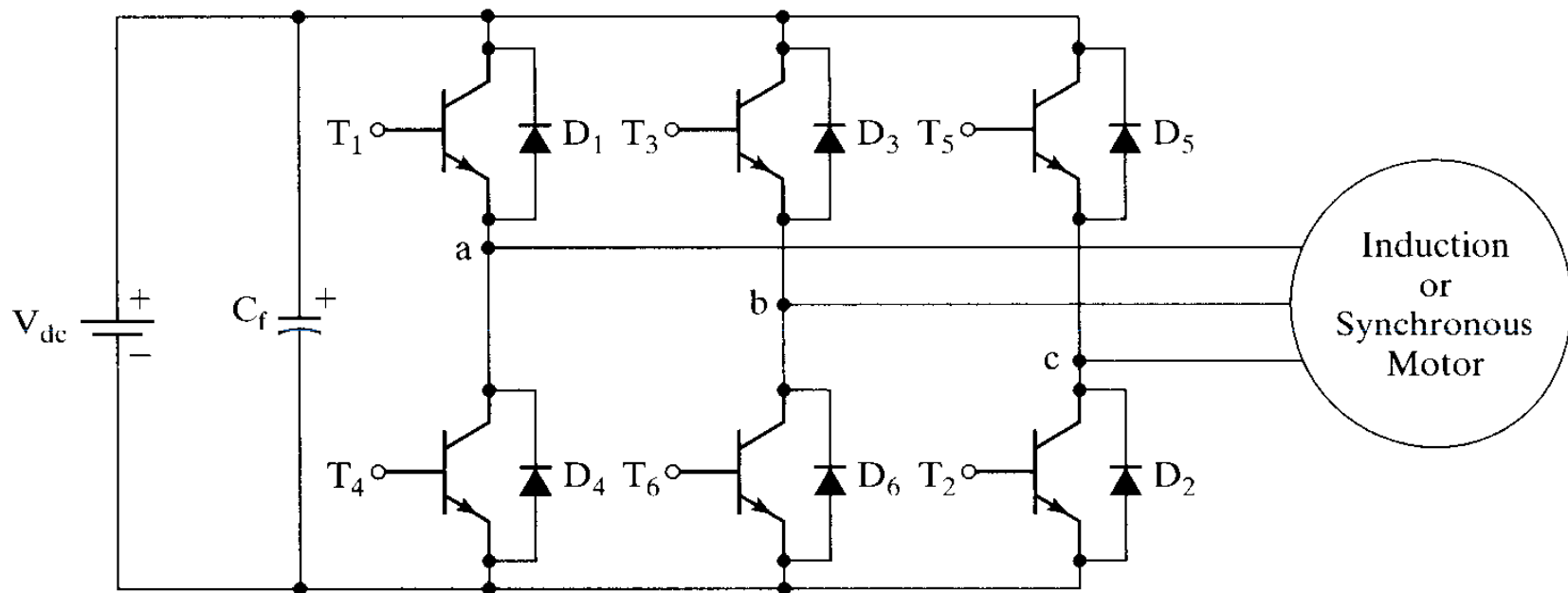


Figure 7.11 Voltage-source inverter with transistors

7.4 Voltage-source inverter

- A generic self-commutating inverter


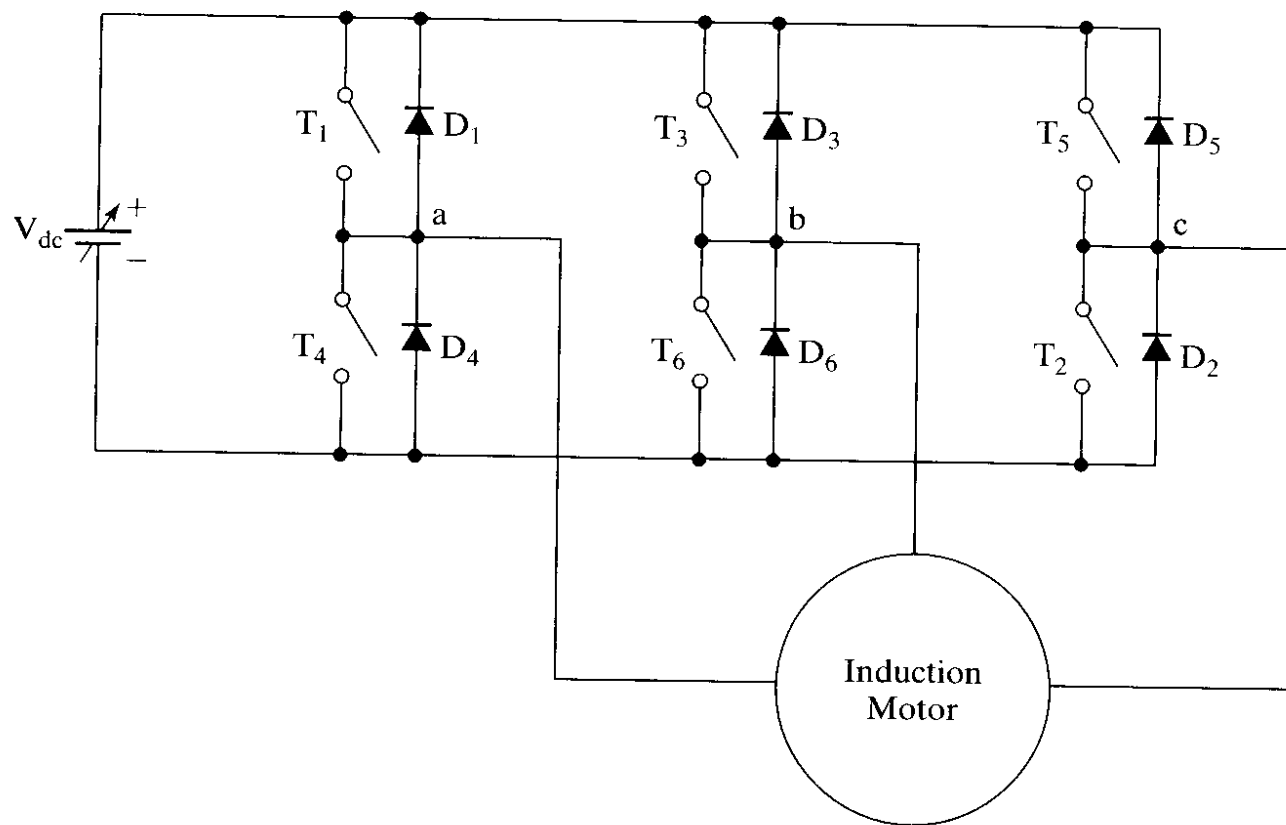


Figure 7.12 A schematic of the generic inverter-fed induction motor drive

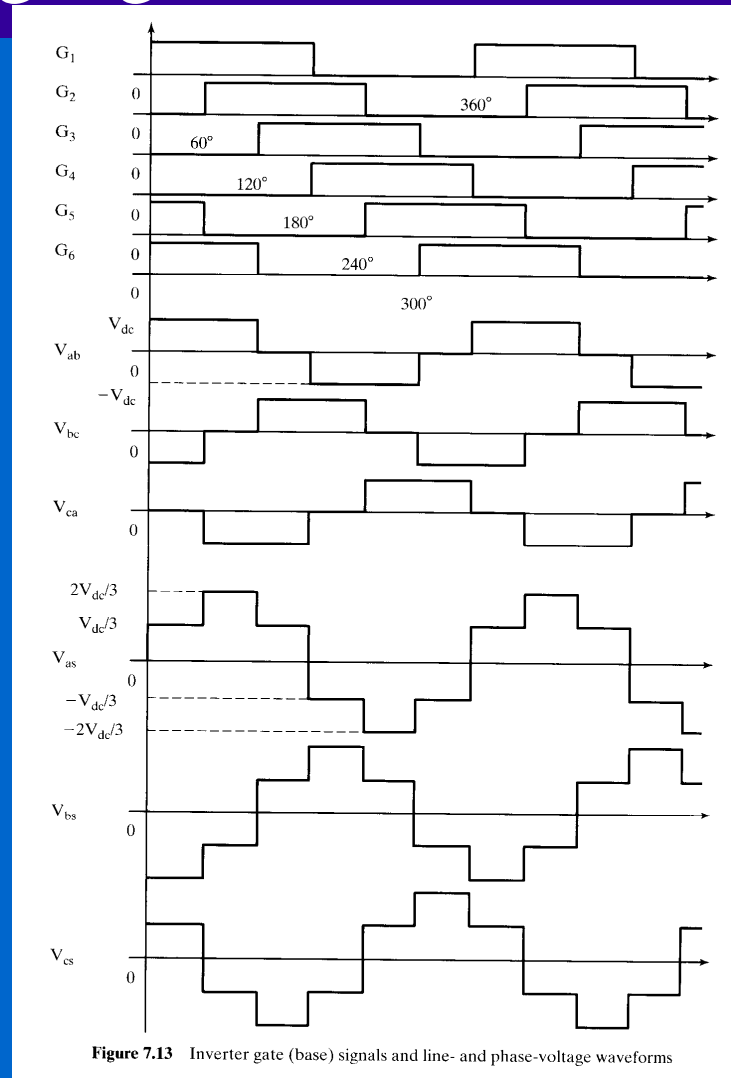- The gating signals and the line voltage



-
-
-

- The line voltage in term of the phase voltage

$$V_{ab} = V_{as} - V_{bs}$$

$$V_{bc} = V_{bs} - V_{cs}$$

$$V_{ca} = V_{cs} - V_{as}$$

- We can obtain

$$V_{ab} - V_{ca} = 2V_{as} - (V_{bs} + V_{cs})$$

- Because a three-phase system is balance,

$$V_{as} + V_{bs} + V_{cs} = 0.$$

-
-
-

- Then, we have

$$V_{ab} - V_{ca} = 3V_{as}$$

- That is,

$$V_{as} = (V_{ab} - V_{ca})/3$$

- Similarly,

$$V_{bs} = (V_{bc} - V_{ab})/3$$

$$V_{cs} = (V_{ca} - V_{bc})/3$$

•
•
•

- These periodic voltage waveforms (in Fourier components) have the following

$$v_{ab}(t) = \frac{2\sqrt{3}}{\pi} v_{dc} (\sin \omega_s t - \frac{1}{5} \sin 5\omega_s t + \frac{1}{7} \sin 7\omega_s t - \dots)$$

$$v_{bc}(t) = \frac{2\sqrt{3}}{\pi} v_{dc} \{ \sin(\omega_s - 120^\circ)t - \frac{1}{5} \sin(5\omega_s - 120^\circ)t + \frac{1}{7} \sin(7\omega_s t - 120^\circ) - \dots$$

$$v_{ca}(t) = \frac{2\sqrt{3}}{\pi} v_{dc} \{ \sin(\omega_s + 120^\circ)t - \frac{1}{5} \sin(5\omega_s + 120^\circ)t + \frac{1}{7} \sin(7\omega_s t + 120^\circ) - \dots$$

- The fundamental rms phase voltage for the six-stepped waveform is

$$V_{ph} = \frac{V_{as}}{\sqrt{2}} = \frac{2}{\pi} \cdot \frac{V_{dc}}{\sqrt{2}} = 0.45 V_{dc}$$

-
-
-

- 7.4.2 Real power

$$P_i = V_{dc}I_{dc} = 3V_{ph}I_{ph}\cos\phi_1$$

$$\Rightarrow I_{dc} = 1.35I_{ph}\cos\phi_1$$

- 7.4.3 Reactive power

$$Q_i = 3V_{ph}I_{ph}\sin\phi_1$$

- 7.4.4 Speed control

- The air gap induced emf

$$E_1 = 4.44k_{\omega 1}\phi_m f_s T_1$$

-
-
-

- Neglecting the stator impedance, $R_s + jX_{1s}$

$$V_{ph} \cong E_1$$

- The flux is then written as

$$\phi_m \cong \frac{V_{ph}}{K_b f_s}$$

$$\text{where } K_b = 4.44 k_{\omega 1} T_1$$

- If K_b is constant

$$\phi_m \propto \frac{V_{ph}}{f_s} \propto K_{vf}$$

-
-
-

- A number of control strategies about the voltage-to-frequency ratio:

- (i) Constant volts/Hz control
- (ii) Constant slip-speed control
- (iii) Constant air gap flux control
- (iv) Vector control

- 7.4.5 Constant volts/Hz control

- Relationship between voltage and frequency

$$V_{as1} = E_1 + I_{s1}(R_s + jX_{1s})$$

-
-
-
- Equivalent circuit of the induction motor

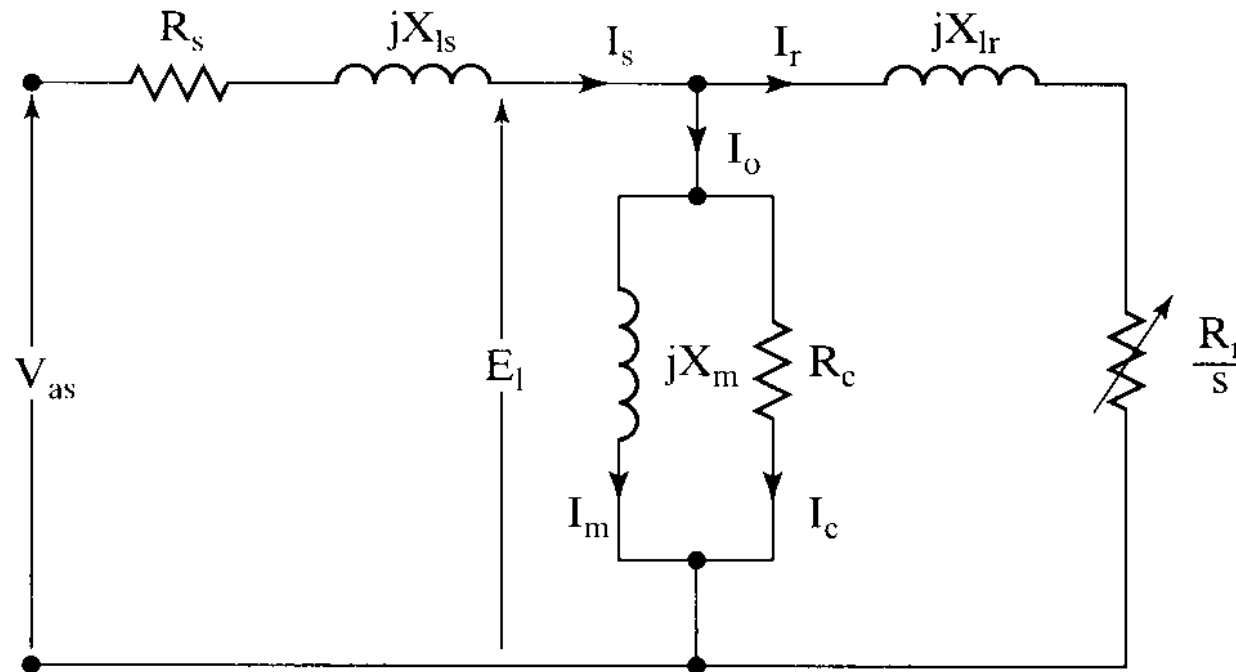


Figure 7.14 Equivalent circuit of the induction motor

-
-
-

- The phase voltage in p.u.

$$V_{asn} = E_{1n} + I_{s1n}(R_{sn} + jX_{1sn})$$

- The p.u. fundamental input voltage

$$V_{asn} = I_{sn}R_{sn} + j\omega_{sn}(\lambda_{mn} + L_{1sn}I_{sn}) \text{ (p.u.)}$$

- The normalized input-phase stator voltage

$$V_{asn} = \sqrt{(I_{sn}R_{sn})^2 + \omega_{sn}^2(\lambda_{mn} + L_{1sn}I_{sn})^2} \text{ (p.u.)}$$

- The relationship between the applied phase voltage and frequency (for law performance)

$$V_{as} = V_o + K_{vk}f_s$$

$$\text{where } V_o = I_{s1}R_s$$

-
-
-

- Because of

$$V_{as} = 0.24V_{dcn}, V_{on} = V_o/V_b, \text{ and}$$

$$E_{1n} = E_1/V_b = K_{vf}f_s/K_{vf}f_b = f_{sn},$$

we have

$$V_{dcn} = 2.22\{V_{on} + f_{sn}\}$$

-
-
-
- Implementation of volts/Hz strategy

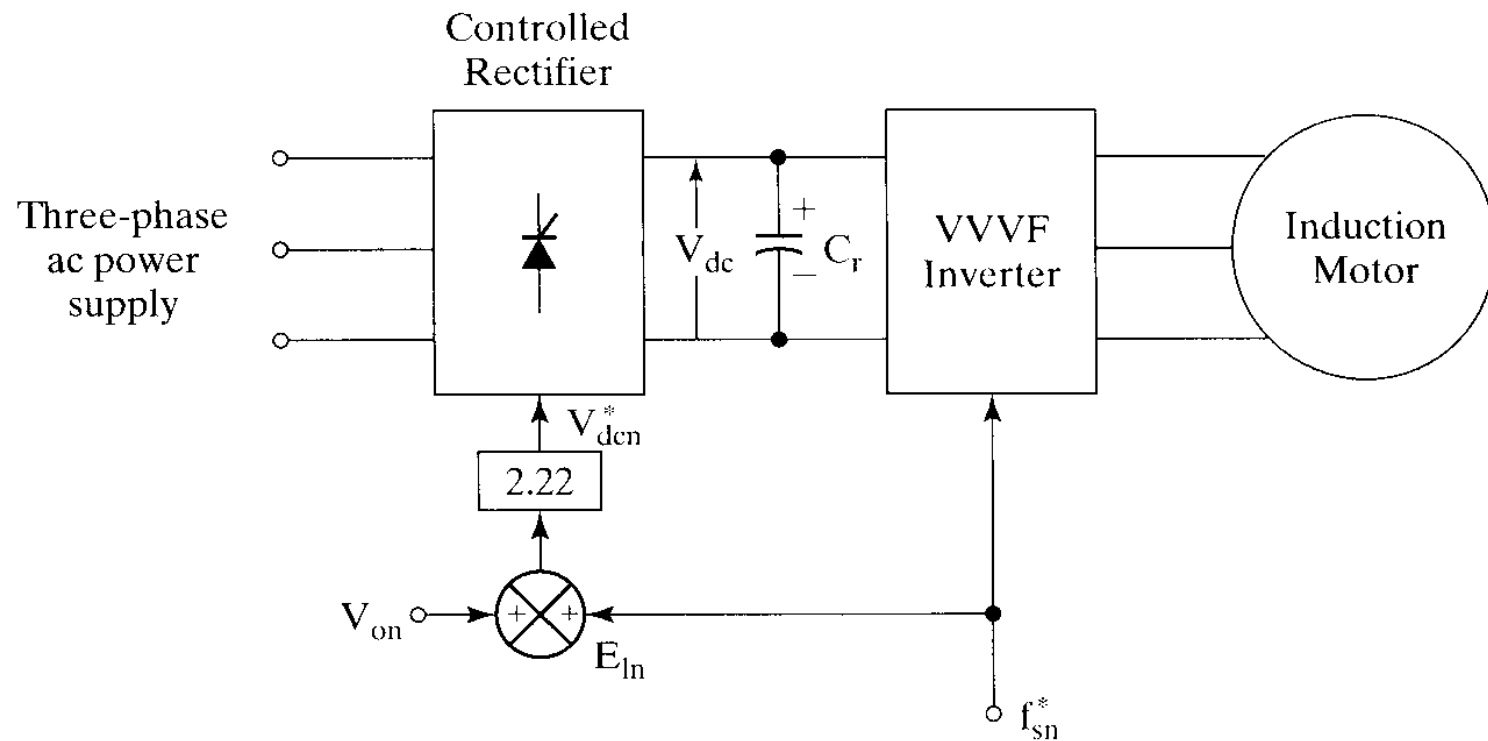


Figure 7.17 Implementation of volts/Hz strategy in inverter-fed induction motor drives

- Closed-loop induction motor drive constant volts/Hz control strategy

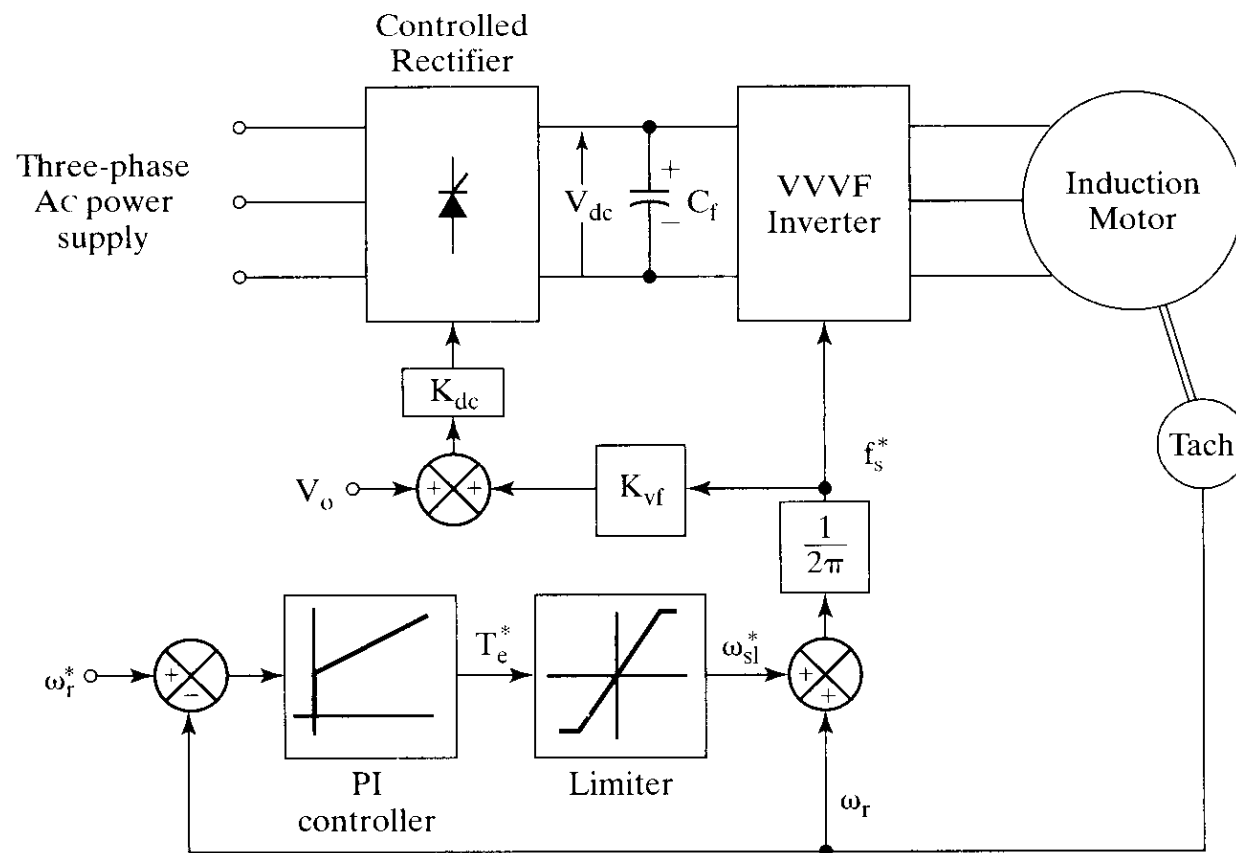


Figure 7.18 Closed-loop induction motor drive with constant volts/Hz control strategy

-
-
-

- 7.4.6 Constant slip-speed control

- Places the drive operation on the static torque-speed characteristic
- The speed of the induction motor

$$\omega_s = \omega_r + \omega_{s1}$$

- The slip is obtained as

$$s = \frac{\omega_{s1}}{\omega_s} = \frac{\omega_{s1}}{\omega_r + \omega_{s1}}$$

- Constant-slip-speed strategy(one-quadrant)

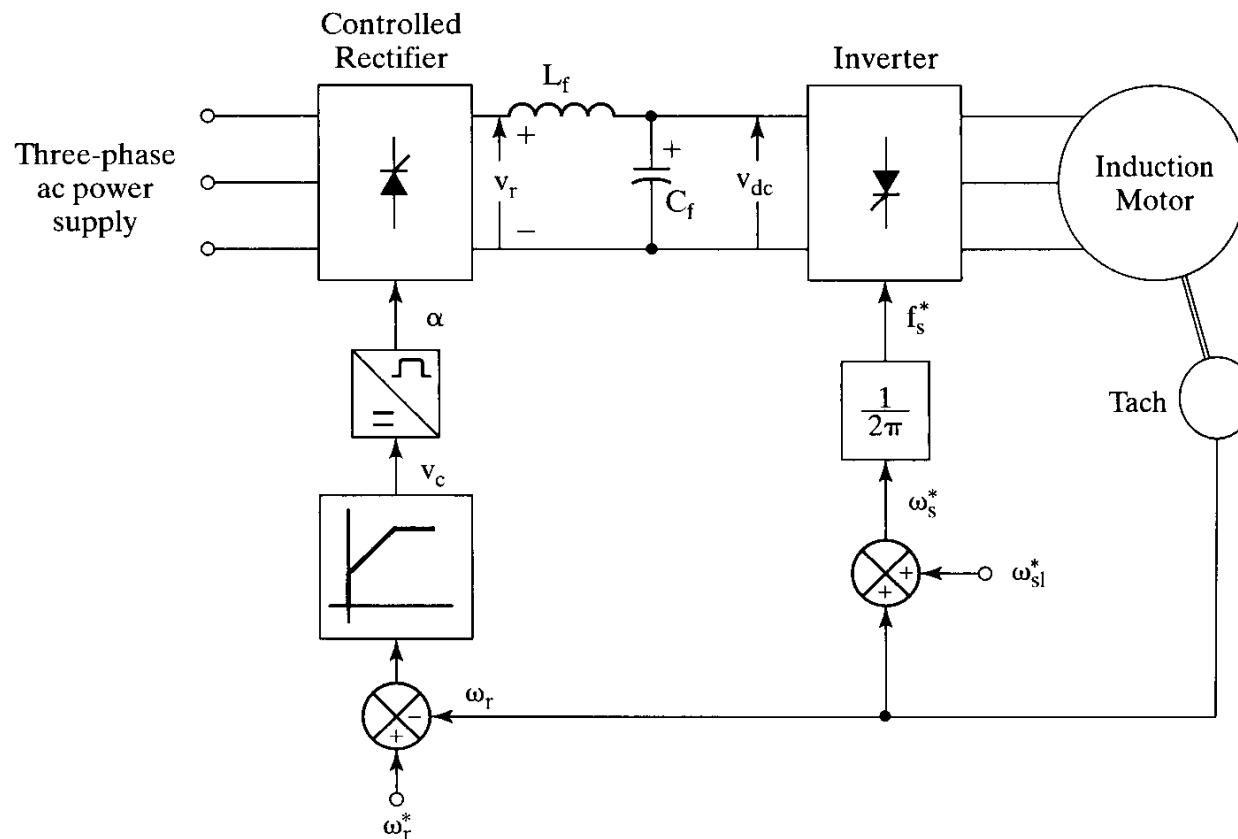


Figure 7.26 Constant-slip-speed drive strategy

- Simplified equivalent circuit considered for the steady state analysis

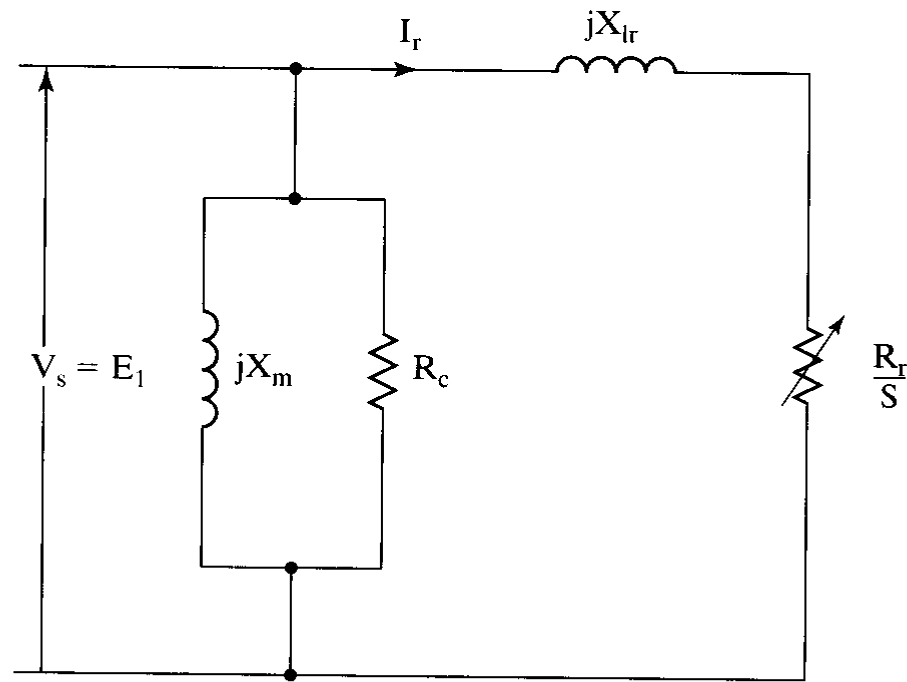


Figure 7.27 Simplified equivalent circuit considered for the steady-state analysis of the slip-controlled induction motor drive

-
-
-
- The rotor current

$$I_r = \frac{E_1}{(\frac{R_r}{s} + jX_{lr})} = \frac{E_1 / \omega_s}{(\frac{R_r}{\omega_{s1}} + jL_{lr})}$$

- The electromagnetic torque

$$T_e = \frac{P}{2} \cdot \frac{P_a}{\omega_s} = 3 \cdot \frac{P}{2} \cdot \frac{I_r^2 R_r}{s \omega_s} = 3 \cdot \frac{P}{2} \cdot \frac{I_r^2 R_r}{\omega_{s1}}$$

$$T_e = 3 \cdot \frac{P}{2} \cdot \frac{E_1^2}{\omega_s^2} \cdot \frac{(\frac{R_r}{\omega_{s1}})}{(\frac{R_r}{\omega_{s1}})^2 + (L_{lr})^2} = K_{tv} \left(\frac{E_1^2}{\omega_s^2} \right) \cong K_{tv} \left(\frac{V_s}{\omega_s} \right)^2$$

$$K_{tv} = \frac{3 \frac{P}{2} \left(\frac{R_r}{\omega_{s1}} \right)}{\left(\frac{R_r}{\omega_{s1}} \right)^2 + (L_{lr})^2}$$

- Torque vs. applied voltage for various slip speed

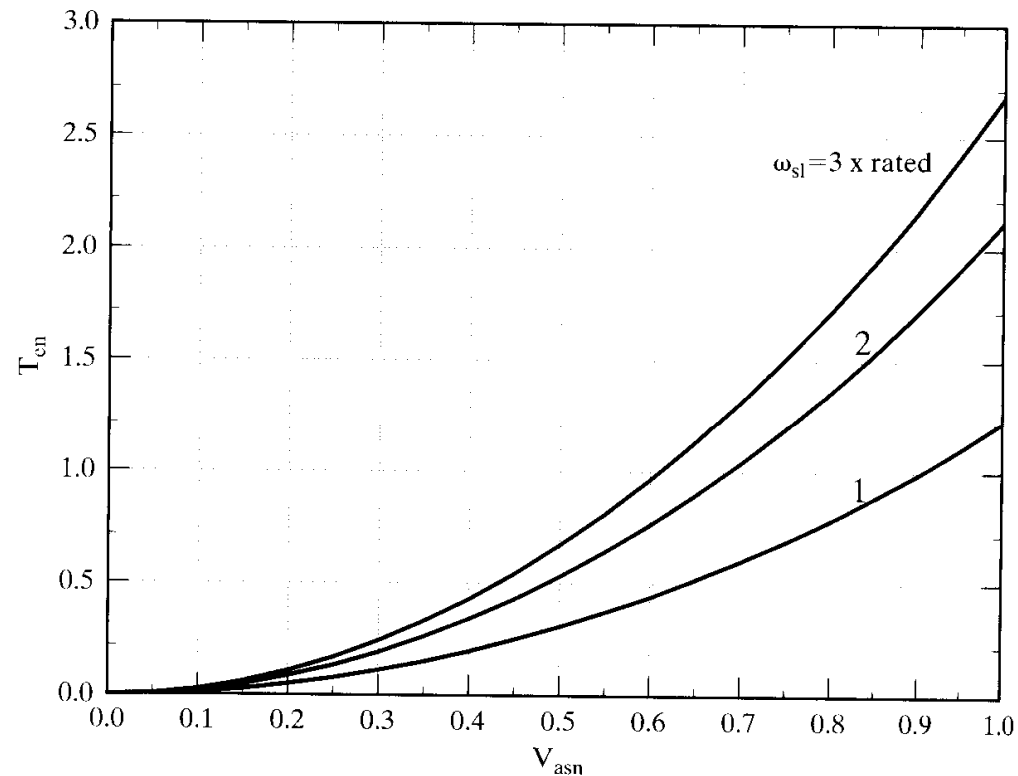


Figure 7.28 Torque vs. applied voltage for various slip speeds at rated stator frequency in p.u.

-
-
-

- 7.4.7 Constant air gap flux control

- Equivalent separately-excited dc motor in terms of its speed but not in terms of decoupling of flux and torque channel.

- Constant air gap flux linkages

$$\lambda_m = L_m i_m = \frac{E_1}{\omega_s}$$

- The electromagnetic torque

$$T_e = 3 \cdot \frac{P}{2} \cdot \lambda_m^2 \cdot \frac{\left(\frac{R_r}{\omega_{s1}}\right)}{\left(\frac{R_r}{\omega_{s1}}\right)^2 + (L_{lr})^2} = K_{tm} \frac{\left(\frac{R_r}{\omega_{s1}}\right)}{\left(\frac{R_r}{\omega_{s1}}\right)^2 + (L_{lr})^2}$$

- Drive strategy for constant-air gap-flux-controlled induction motor drive



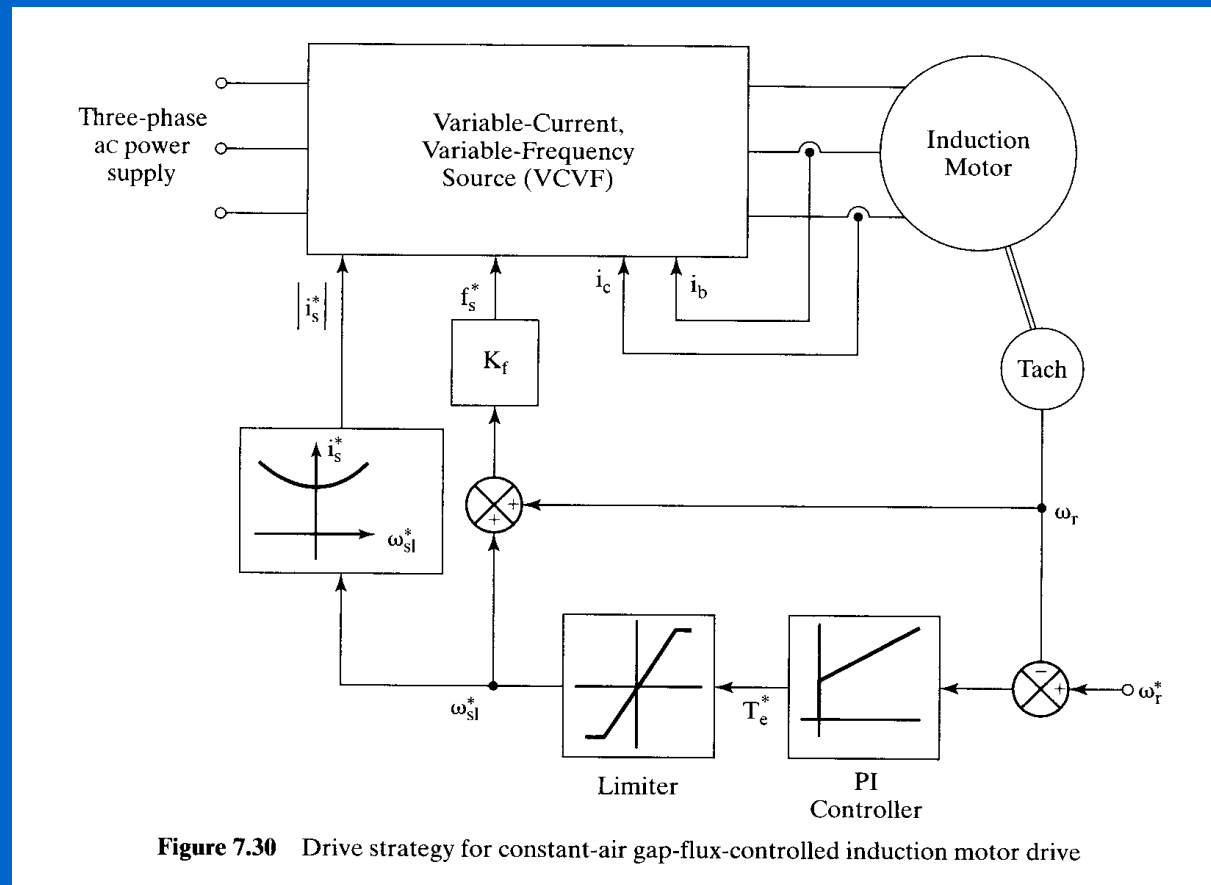
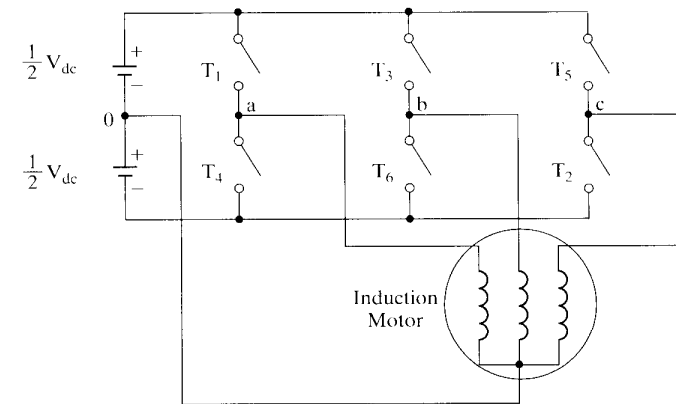


Figure 7.30 Drive strategy for constant-air gap-flux-controlled induction motor drive

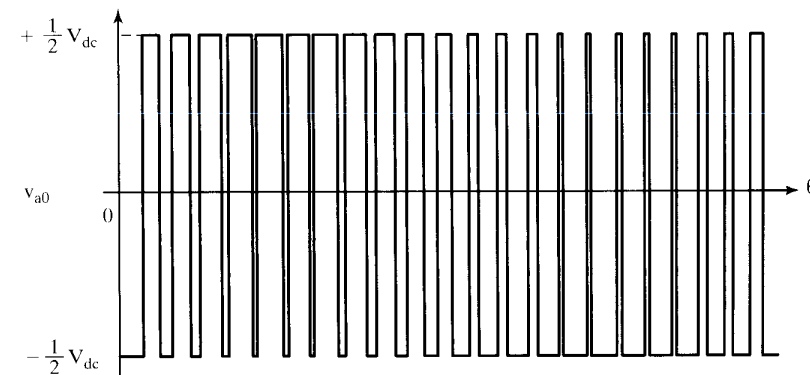-
-
-
- 9.4.7 Control of harmonics
- Sinusoidal pulse-width modulation



(i) Inverter motor schematic

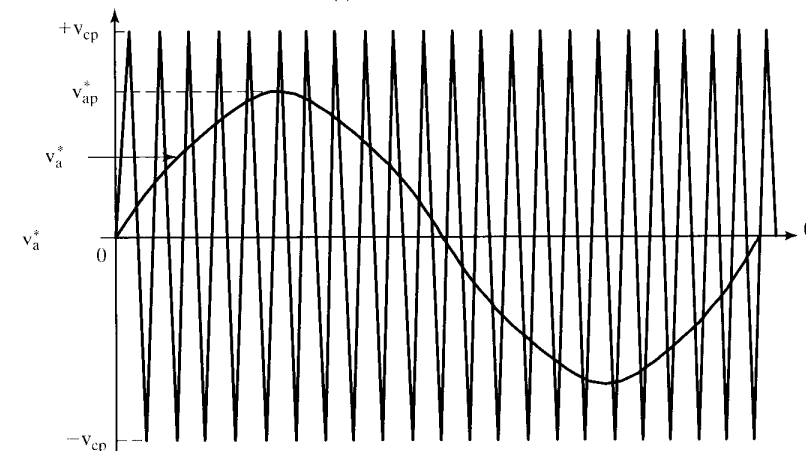

(ii) PWM operation

Figure 7.37 Sinusoidal pulse-width modulation

-
-
-

- The switching logic for one phase

$$\begin{aligned} v_{a0} &= \frac{1}{2} V_{dc}, & v_c < v_a^* \\ &= -\frac{1}{2} V_{dc}, & v_c > v_a^* \end{aligned}$$

- The fundamental of this midpoint voltage

$$v_{a01} = \frac{V_{dc}}{2} \cdot \frac{v_{ap}^*}{v_{cp}}$$

-
-
-

- 7.4.10 Steady-state evaluation with PWM voltage

- PWM voltage generation

$$t(i) = \frac{1 \pm m \sin[a(i)]}{2f_c}, \quad + \text{ for even } n; - \text{ for odd } n$$

$$a(i) = \frac{2\pi i}{n}, \text{ rad};$$

where n is the ratio between the carrier and modulation frequencies, $t(i)$ is i th pulse width, m is the modulation ration, f_c is the carrier frequency.

-
-
-

- The pulse widths in electrical radians

$$p_w(i) = t(i)f_s, \text{ rad}$$

where f_s is the modulation frequency.

- (see the table on pp. 370)
- The d and q axes voltages

$$v_{qs} = \frac{2}{3} [v_{as} - 0.5(v_{bs} + v_{cs})]$$

$$v_{ds} = \frac{1}{\sqrt{3}} [(v_{cs} - v_{bs})]$$

- The model in the stator reference frames

$$\mathbf{V} = (\mathbf{R} + \mathbf{L}p)\mathbf{i} + \mathbf{G}\omega_r\mathbf{i}$$

$$\mathbf{V} = [v_{as} \ v_{ds} \ 0 \ 0]^t$$

$$\mathbf{i} = [i_{qs} \ i_{ds} \ i_{qr} \ i_{dr}]^t$$

$$\mathbf{R} = \begin{bmatrix} R_s & 0 & 0 & 0 \\ 0 & R_s & 0 & 0 \\ 0 & 0 & R_r & 0 \\ 0 & 0 & 0 & R_r \end{bmatrix}$$

$$\mathbf{L} = \begin{bmatrix} L_s & 0 & L_m & 0 \\ 0 & L_s & 0 & L_m \\ L_m & 0 & R_r & 0 \\ 0 & L_m & 0 & R_r \end{bmatrix}$$

$$\mathbf{G} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & L_m & 0 & -L_r \\ -L_m & 0 & L_r & 0 \end{bmatrix}$$

-
-
-

- State-space form

$$\dot{X} = AX + Bu$$

$$\text{where } A = -L^{-1}[R + \omega_r G]$$

$$B = L^{-1}$$

$$X = i$$

$$u = V$$

-
-
-

- Direct evaluation of steady-state current

- The solution of current vector

$$X(t) = e^{At}X(0) + \int_0^t e^{A(t-\tau)}Bu(\tau)d\tau$$

- Discretization

$$X(T_s) = e^{AT_s}X(0) + (e^{AT_s} - I)A^{-1}Bu(0)$$

- The k^{th} sampling interval

$$X(k+1) = \Phi X(k) + Fu(k)$$

$$\text{where } \Phi = e^{AT_s} \text{ and } F = (\Phi - I)A^{-1}B$$

-
-
-

- $X(k+1) = X(0)$ (if $k+1 = 360$ electrical degrees)

- The steady-state initial vector

$$X(0) = [I - \Phi^{(k+1)}]^{-1} \{ \sum_{j=0 \dots k} \Phi^j F u(k-j) \}$$

- Steady-state performance

$$T_e(k) = \frac{3}{2} \frac{P}{2} L_m \{ i_{qs}(k) i_{ds}(k) - i_{ds}(k) i_{qr}(k) \}$$

$$i_{as}(k) = i_{qs}(k)$$

$$i_{bs}(k) = -0.5 i_{qs}(k) - 0.866 i_{ds}(k)$$

•
•
•

7.5 Current-source ...

- Torque is directly related to the current rather than voltage.
- 7.5.2 ACSI (Autosequentially commutated Current-source Inverter)
- The inductor is provided to maintain the dc link current at a steady value.

-
-
-
- Current-source induction motor drive

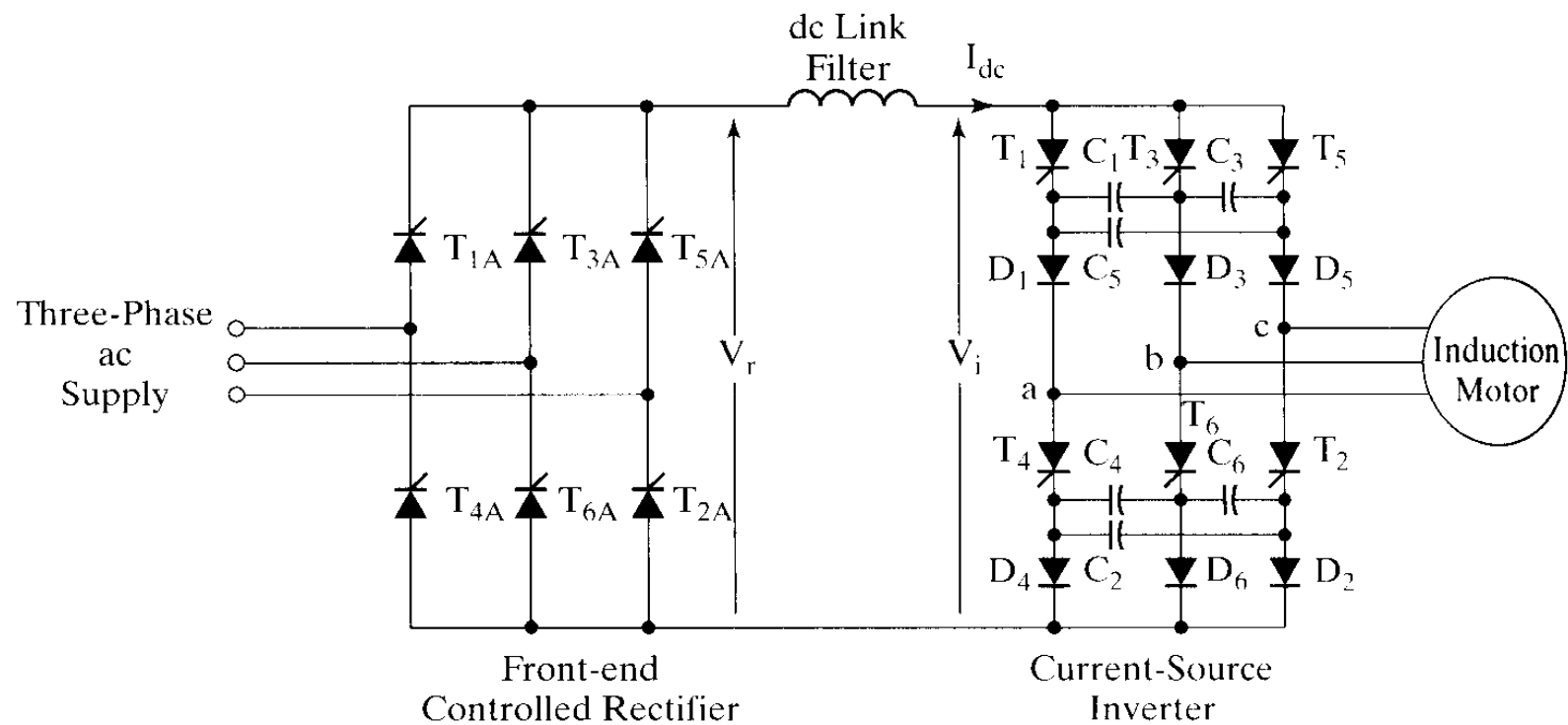


Figure 7.44 Current-source induction motor drive

- Commutation

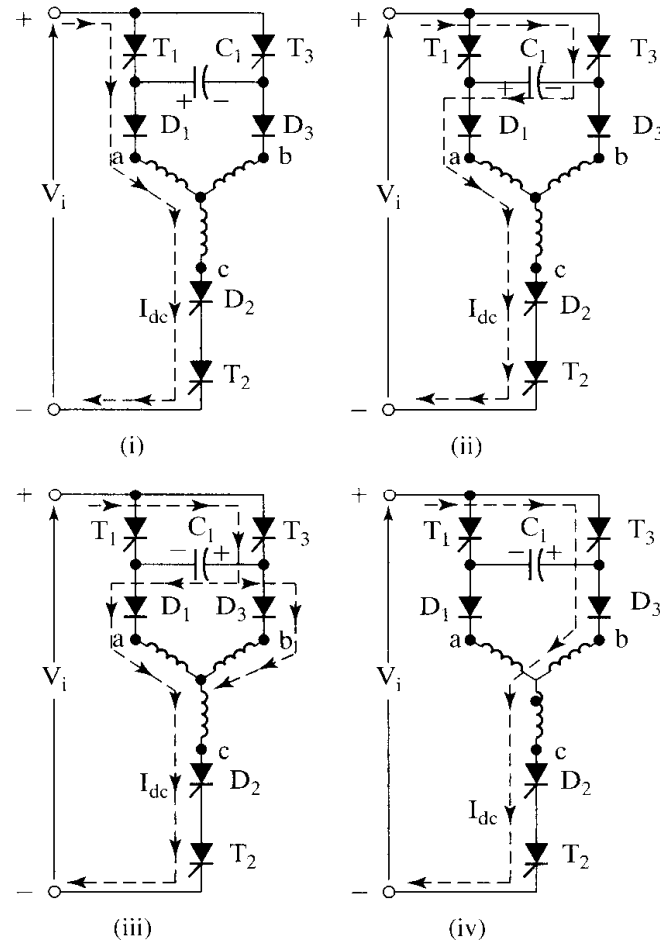


Figure 7.45 Commutation sequence in an autosequentially commutated current-source inverter

-
-
-
- Stator current in a star connection

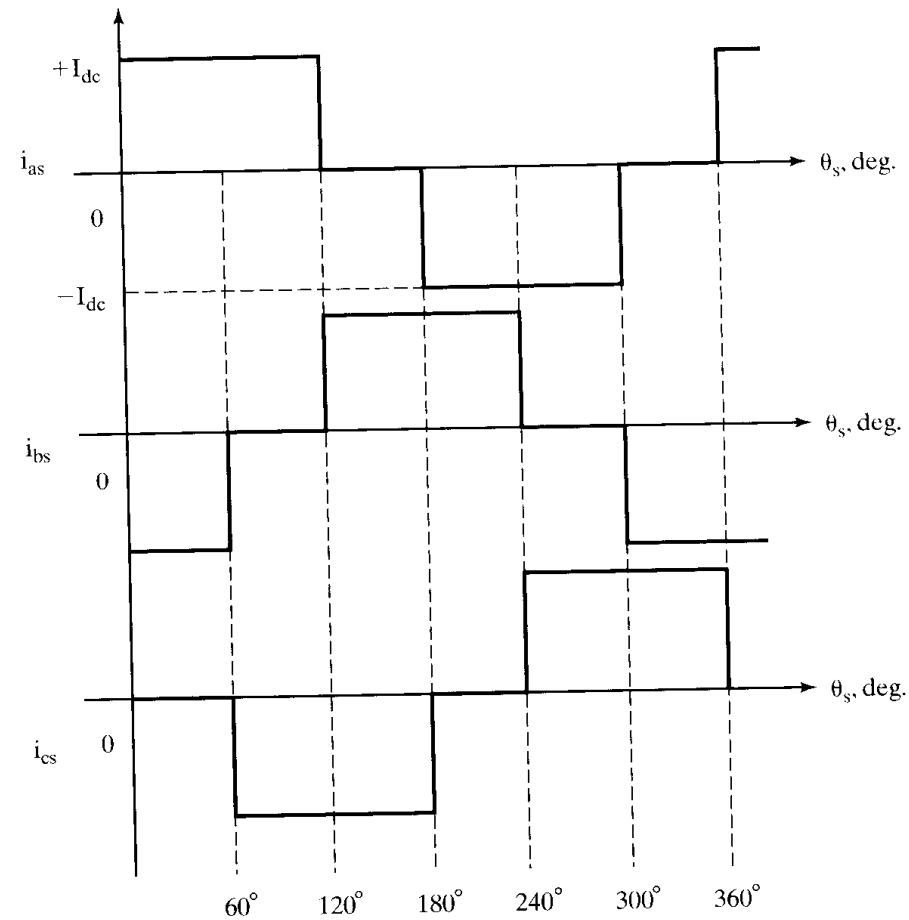


Figure 7.46 Stator currents in a star-connected induction motor fed from a current source

- Forward motoring

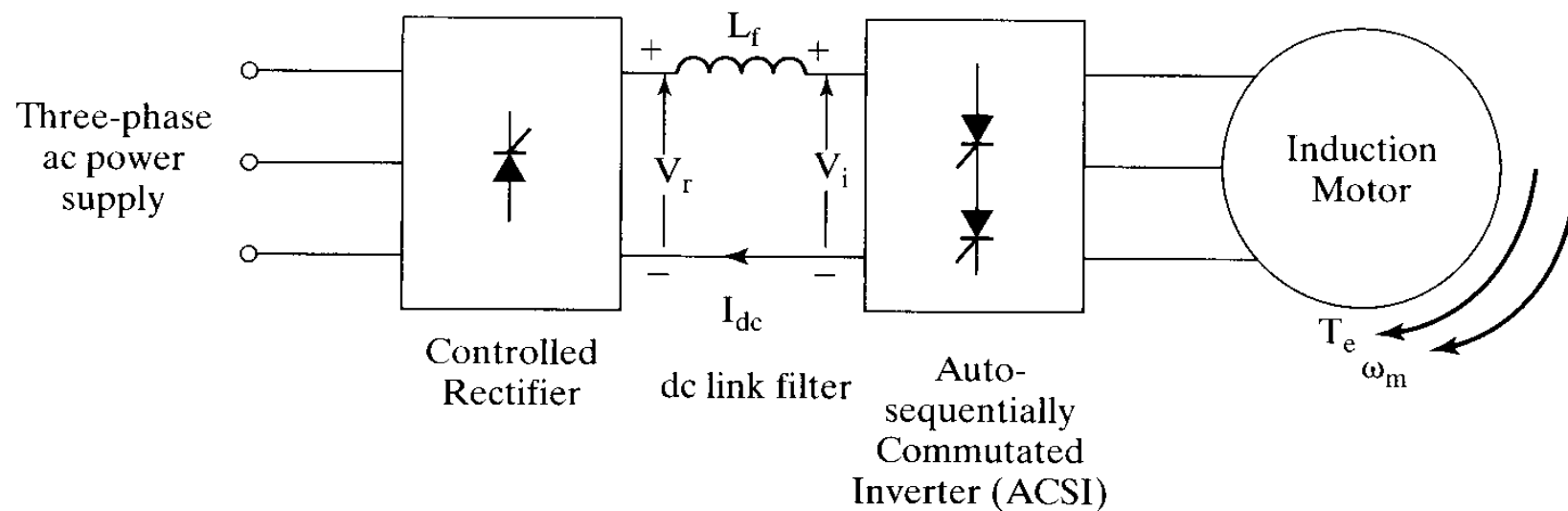


Figure 7.47 Forward motoring of the current-source induction motor drive

-
-
-
- Regeneration

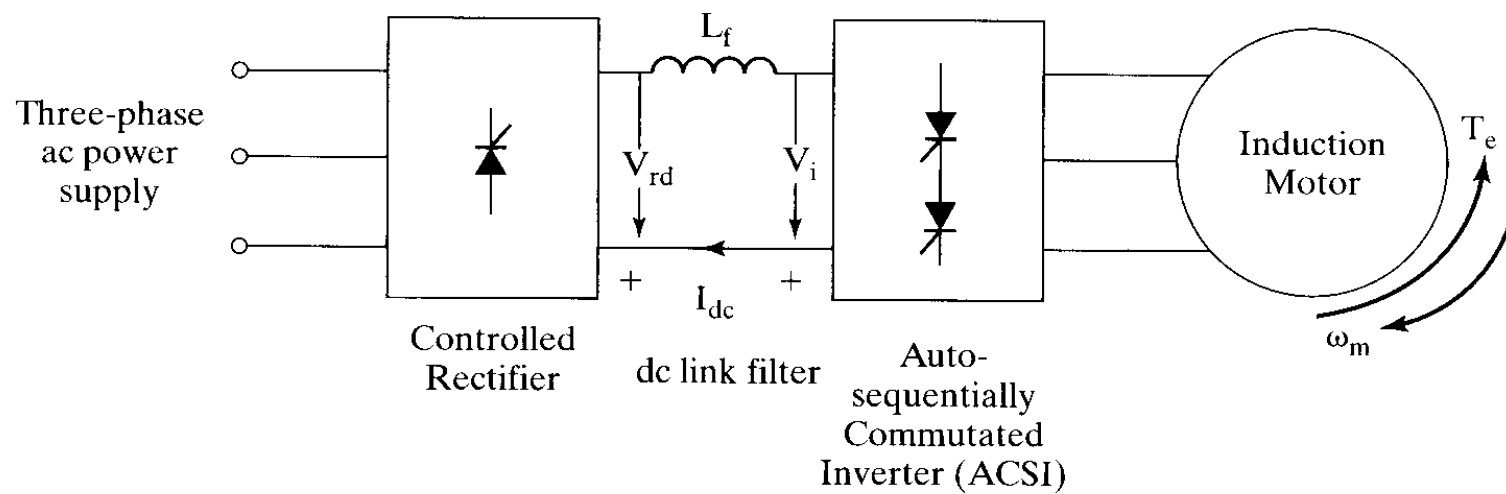


Figure 7.48 Regeneration in the current-source induction motor drive

-
-
-
- 7.5.3 Steady-state performance
- Equivalent circuit approach

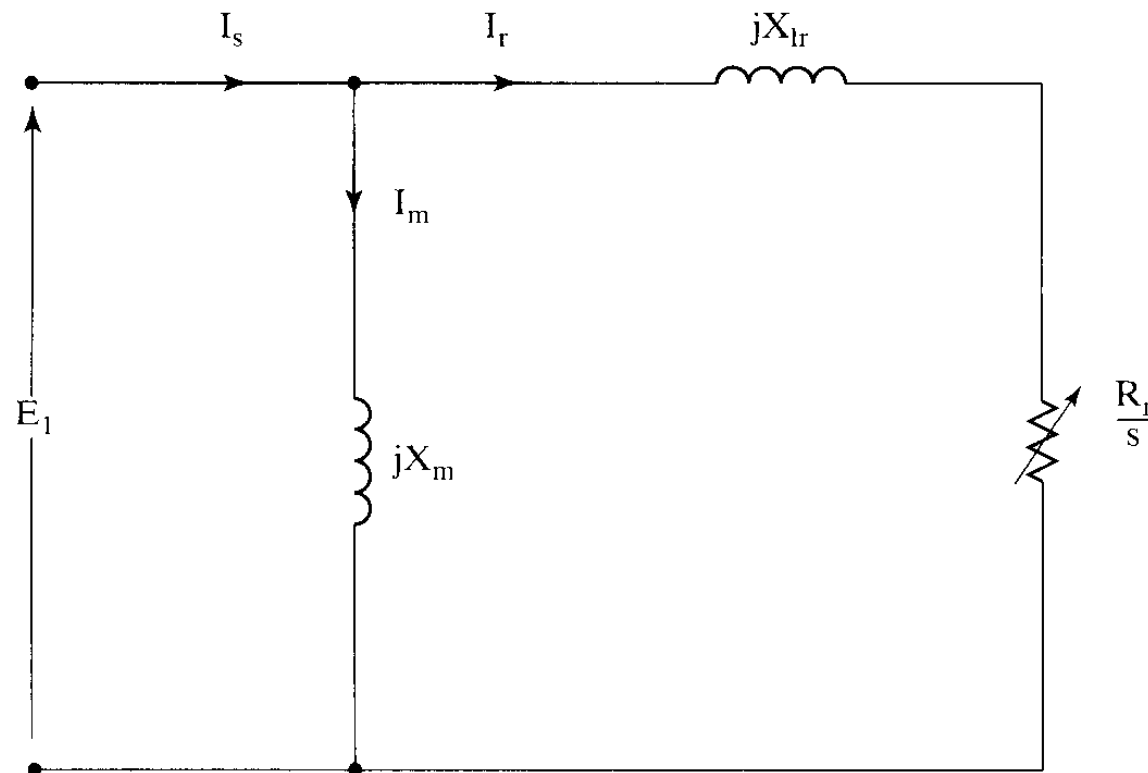


Figure 7.49 Induction-motor equivalent circuit with constant stator current

-
-
-
- The rotor and magnetizing currents

$$I_r = \frac{jL_m}{\frac{R_r}{s\omega_s} + jL_r} \cdot I_s$$

$$I_m = \frac{\frac{R_r}{s\omega_s} + jL_{lr}}{\frac{R_r}{s\omega_s} + jL_r} \cdot I_s$$

where $I_s \frac{\sqrt{2}\sqrt{3}}{\pi} I_{dc} = 0.779 I_{dc}$

- The electromagnetic torque

$$T_e = 3 \cdot \frac{P}{2} \cdot \frac{L_m^2}{\left(\frac{R_r}{s\omega_s}\right)^2 + L_r^2} \cdot \frac{R_r}{s\omega_s} \cdot I_s^2$$

-
-
-

- The maximum torque occurs at

$$s = R_r / \omega_s L_r$$

- Thus

$$T_{e(\max)} = \frac{3}{2} \cdot \frac{P}{2} \cdot \frac{L_m^2}{\left(\frac{R_r}{s\omega_s}\right)} \cdot I_s^2 = \frac{3}{2} \cdot \frac{P}{2} \cdot \frac{L_m^2}{L_r} \cdot I_s^2$$

- 7.5.4 Direct steady-state evaluation of six-step current-source inverter-fed induction motor (CSIM) drive system

-
-
-
- Stator currents:

(i) interval I: $0 < \theta_s < 60^\circ$

$$i_{as} = I_{dc}; \quad i_{bs} = -I_{dc}; \quad i_{cs} = 0.$$

The quadrature axis stator current

$$i_{qs}^e = \frac{2}{3} [i_{as} \cos \theta_s + i_{bs} \cos(\theta_s - \frac{2\pi}{3}) + i_{cs} \cos(\theta_s + \frac{2\pi}{3})]$$

$$i_{qsI}^e = a I_{dc} \cos(\theta_s + \frac{\pi}{6}) \quad \text{where} \quad a = \frac{2}{\sqrt{3}}$$

similarly,

$$i_{dsI}^e = a I_{dc} \sin(\theta_s + \frac{\pi}{6})$$

-
-
-

(ii) interval II: $60^\circ < \theta_s < 120^\circ$

The quadrature and direct axis stator currents

$$i_{qsII}^e = aI_{dc} \cos(\theta_s - \frac{\pi}{6}) = aI_{dc} \cos(\theta_s + \frac{\pi}{6} - \frac{\pi}{3}) = \frac{1}{2}i_{qsI}^e + \frac{\sqrt{3}}{2}i_{dsI}^e$$

$$i_{dsII}^e = aI_{dc} \sin(\theta_s - \frac{\pi}{6}) = aI_{dc} \sin(\theta_s + \frac{\pi}{6} - \frac{\pi}{3}) = -\frac{\sqrt{3}}{2}i_{qsI}^e + \frac{1}{2}i_{dsI}^e$$

- The transformation matrix

$$\begin{bmatrix} i_{qs}^e(\theta_s + \frac{\pi}{3}) \\ i_{ds}^e(\theta_s + \frac{\pi}{3}) \end{bmatrix} = \begin{bmatrix} \frac{1}{2} & \frac{\sqrt{3}}{2} \\ -\frac{\sqrt{3}}{2} & \frac{1}{2} \end{bmatrix} \begin{bmatrix} i_{qs}^e(\theta_s) \\ i_{ds}^e(\theta_s) \end{bmatrix}$$

•

•

•

 K_{ps}, K_{is}